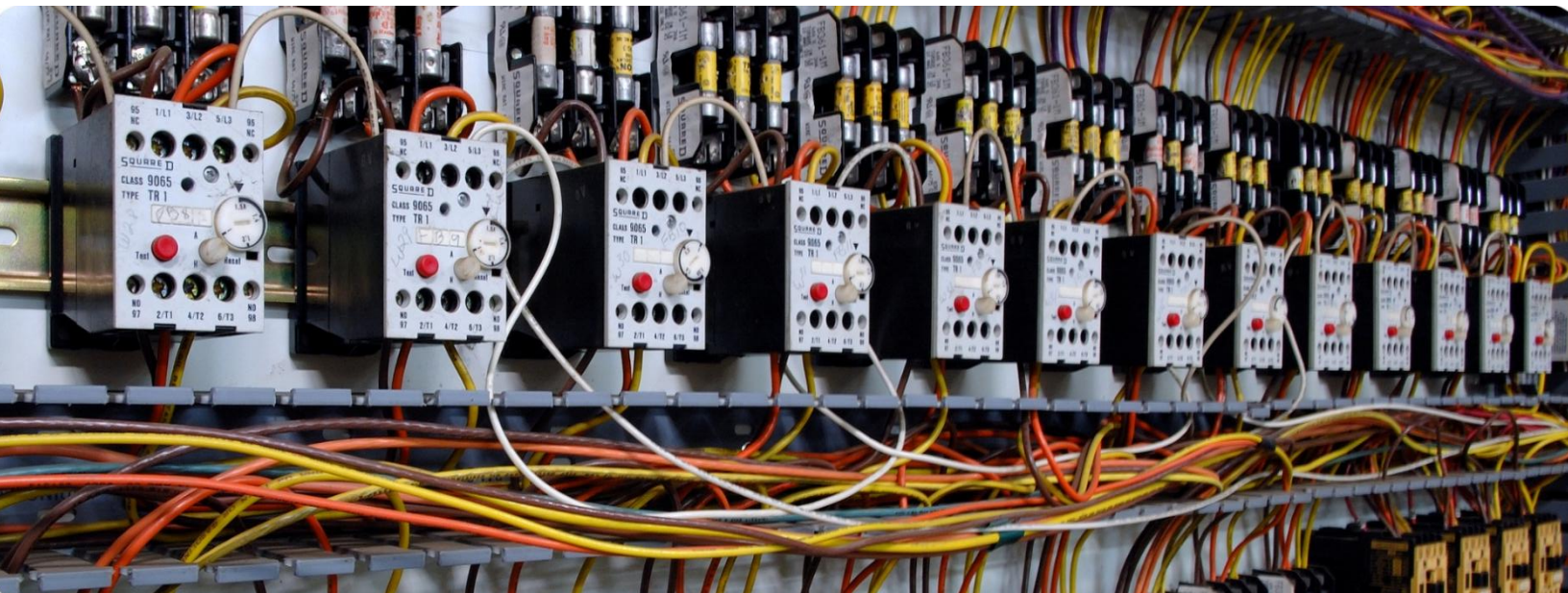


Participant Resource Guide

Electrical Foundations

May 2026



Course Outline

- Module 1: Introduction to Electricity
- Module 2: Basic Electrical Principles
- Module 3: AC and DC Electricity

Module 4: Circuit Components & Architecture

- Module 5: Magnetism and Electromagnetism
- Module 6: Electrical Tools
- Module 7: Safety and PPE



U.S. Department of Transportation
Federal Transit Administration

Course: Electrical Foundations

Version Date: May 2026

This document was prepared by the Transit Workforce Center with the financial assistance of the Federal Transit Administration, U.S. Department of Transportation.

Transit Workforce Center

8403 Colesville Road, Suite 825

Silver Spring, MD 20910

Tel: 855-888-NTWC (6892)

Contact us via email at twc@transportcenter.org

Module 4 – Circuit Components & Architecture

Objectives


- Define basic types of circuits and differences between them.
- Draw and label a simple electrical circuit.
- Define the major components of an electrical circuit and describe their functionality.
- Apply Kirchhoff's Current and Voltage Laws to analyze circuits and solve for unknown electrical values.
- Identify the major symbols for circuit components.
- Recognize basic electrical diagrams.

Key Terms

- Block Diagram
- Capacitor
- Circuit Breaker
- Circuit Protection
- Diode
- Electrical Circuit
- Fuse
- Inductor
- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)
- Load
- One-Line Diagram
- Parallel Circuit
- Power Rating
- Power Source
- Rectifier
- Relay
- Resistance (R)
- Resistor
- Schematic
- Sensor
- Series Circuit
- Series-Parallel Circuit
- Switch
- Tolerance
- Transformers
- Transistor
- Wire

Participant Resource Guide

Circuit Components & Architecture

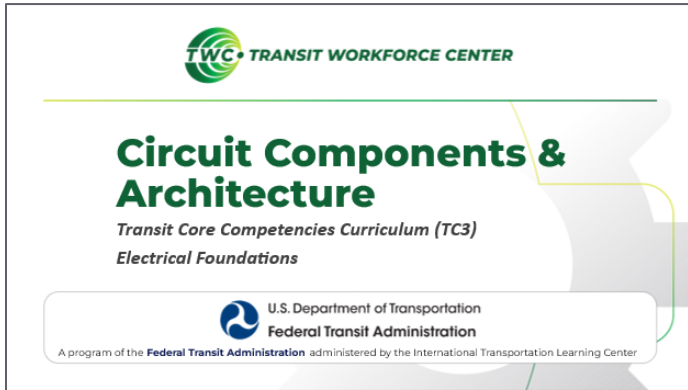


Objectives

- Define basic types of circuits and differences between them.
- Draw and label a simple electrical circuit.
- Define the major components of an electrical circuit and describe their functionality
- Apply Kirchhoff's Current and Voltage Laws to analyze circuits and solve for unknown electrical values.
- Identify the major symbols for circuit components.
- Recognize basic electrical diagrams.

4

Agenda


- Welcome and Warm Up
- Electrical Circuit Design
- Kirchhoff's Laws
- Electrical Circuit Components
- Circuit Diagram Symbols
- Electrical Circuit Diagrams
- Quiz and Wrap Up



5

Warm Up - Review Discussion

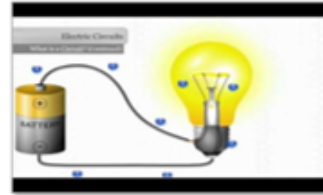- How do the electrons form in this circuit?
- Why wouldn't the light bulb light up if electricity flow is not complete?
- How does electricity flow in a circuit?
- What is a short circuit?




Need a refresher? View this video from Module 1.



Notes:

- Watch the video and answer the following questions:
 1. How do the electrons form in this circuit?
 2. What is a complete circuit?
 3. Why wouldn't the light bulb light up if electricity flow is not complete?
 4. How does electricity flow in a circuit?
 5. What is a short circuit?

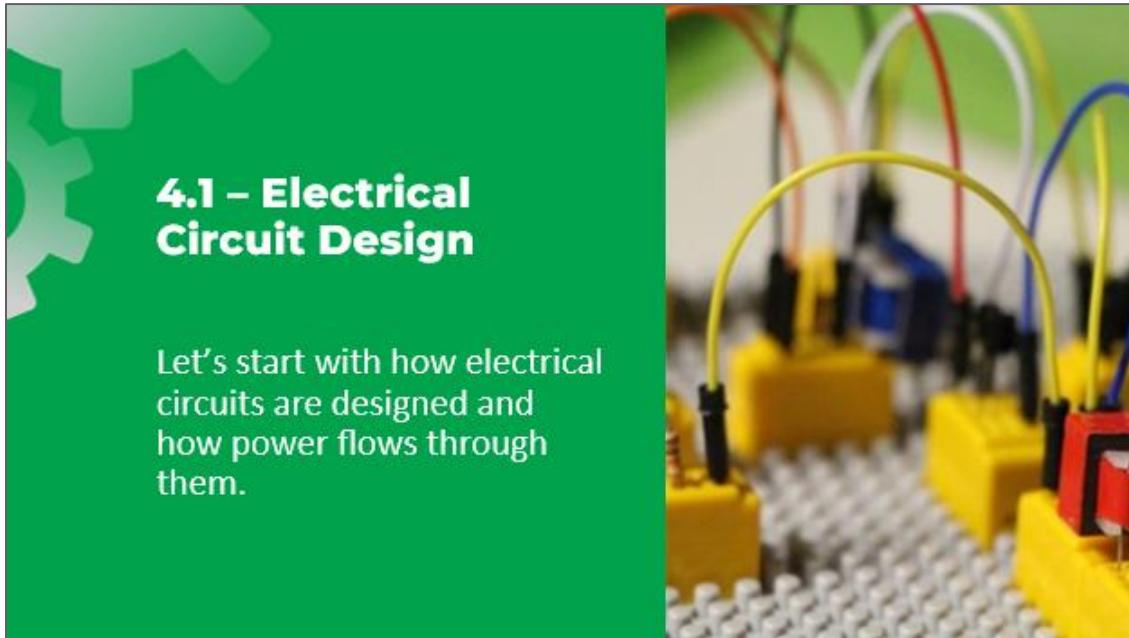Video link: <https://www.youtube.com/watch?v=VnnpLaKsqGU>




Notes:

- In this section, you'll learn about how electrical circuits are designed and how power flows through them.

Electrical Circuit

An unbroken loop of conductive material that allows electrons to flow through the loop continuously

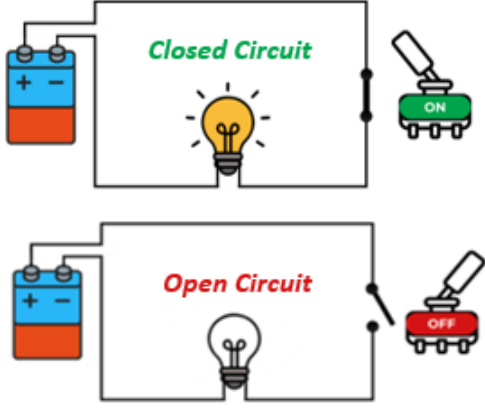- Circuit is **closed** – complete path, electrons *can* flow
- Circuit is **open** – loop is broken, electrons *cannot* flow



The diagram illustrates a Series DC Circuit in two states. In the top state, labeled "Closed Circuit", a battery is connected to a light bulb and a switch that is turned "ON". The light bulb is shown as illuminated. In the bottom state, labeled "Open Circuit", the same battery and light bulb are connected, but the switch is turned "OFF", and the light bulb is not illuminated. The text "Series DC Circuit" is centered below the diagrams.

8


Notes:

- An **electrical circuit** is an unbroken loop of conductive material that allows electrons to flow through the loop continuously.
 - If the **circuit is closed**, there is a complete path meaning electrons *can* flow.
 - If the **circuit is open**, the loop is broken and the electrons cannot flow.
- Check out the images on the slide – they demonstrate the open and closed states.
- You will typically see this in systems powered by batteries, DC power supplies, or rectifiers.
- The voltage level in a DC circuit stays constant over time — unlike alternating current, where it changes direction periodically.
- In a closed circuit, current flows through the intended path — through the load, like the light bulb shown here.
- A **short circuit** can occur when current takes an unintended low-resistance path, bypassing the load or components in the circuit.
 - Instead of flowing *through* the bulb, it takes a shortcut around it.
- In DC circuits, a short circuit can cause a quick increase in current because there is little to slow it down. The sudden spike can cause overheating and fire hazards.
 - That's why protection devices like fuses and circuit breakers are critical in all electrical systems — they interrupt the circuit before damage occurs.
- Basically, any time the hot wire (positive) directly make contact with the neutral/ ground wire (negative) there is a short circuit.

Module 4 – Circuit Components & Architecture

Series Circuits

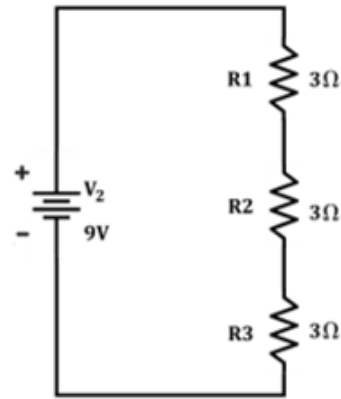- **One path** for current to flow - components connected end-to-end in a single loop
- **Current** = same through all components
- Total **resistance** = sum of all resistances
- **Voltage** divides across each load
- If one component fails, the entire circuit stops working



9


Notes:

- A **series circuit** has only **one path** for current to travel.
- All components are connected **end-to-end in a single loop**, so the same current flows through each component.
- In a series circuit:
 - Current remains constant throughout the circuit.
 - Total resistance is the sum of all individual resistances.
 - Voltage divides across each load based on its resistance.
- Because there is only one path, if one component opens or fails, the entire circuit stops working.

Parallel Circuits

- **Multiple paths** for current to flow — components connected across the same voltage source
- **Voltage** stays the same across each branch
- **Current** divides among the branches
- Total **resistance** is less than the smallest resistor in the circuit


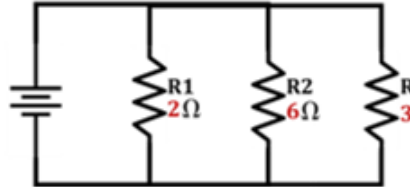
- If one branch fails, the other branches can continue operating



10


Notes:

- A **parallel circuit** has multiple paths for current to flow.
- Instead of being connected end-to-end in one loop, the components are connected across the same voltage source in separate branches.
- In a parallel circuit:
 - Voltage remains the same across each branch.
 - Current divides among the available paths.
 - Total resistance is always less than the smallest individual resistor in the circuit.
- The last point is important — adding branches actually *reduces* overall resistance.
- Because there are multiple paths, if one branch opens or a component fails, the other branches can continue operating. This is why parallel circuits are commonly used in lighting and vehicle electrical systems — one failed component doesn't shut everything down.

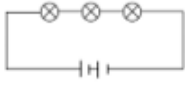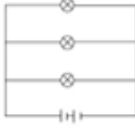Series vs. Parallel Circuits	
Series 	Parallel 
<ul style="list-style-type: none">✓ Only one path for current flow✓ Constant current, resistance adds up, divided voltage✓ If one components fails, whole circuit breaks and stops flow	<ul style="list-style-type: none">✓ Multiple paths for current flow✓ Constant voltage, resistance decreases, divided current✓ If one component fails, has others to continue current flow
11	

Notes:

- **Series:**
 - In a series circuit, there is only one path for current to flow, so the same current moves through every component in the circuit.
 - As you add more components, the total resistance increases and the voltage is shared across them- and if one component fails, the entire circuit opens and current stops everywhere.
- **Parallel:**
 - In a parallel circuit, there are multiple paths for current, which gives the current more than one way to flow through the system.
 - Each branch receives the same voltage, but the current divides between paths, and if one component fails, the rest of the circuit can continue to operate.

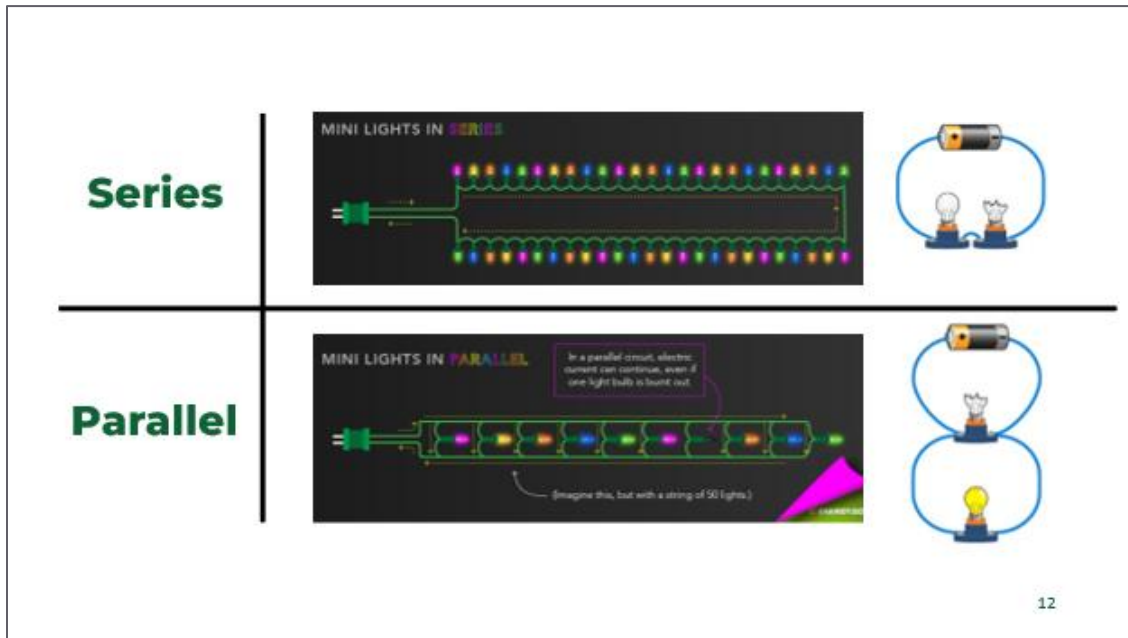


Notes:

- The slide shows a few visual examples of series and parallel circuits.
- On the top row, we have a series circuits. In the holiday light example, if one light goes out then all lights (loads) will go out.
- On the bottom row, we have parallel circuits. If one light goes out the others will remain lit.
- Modern holiday lights usually use a parallel circuit. This way, one light going out does not affect the rest of the string.
- Other instances, as with fire alarms, the use of series circuits is needed. This way if an alarm is triggered in one room of a school for instance, they all go off, giving people time to evacuate safely.

Series-Parallel Circuits

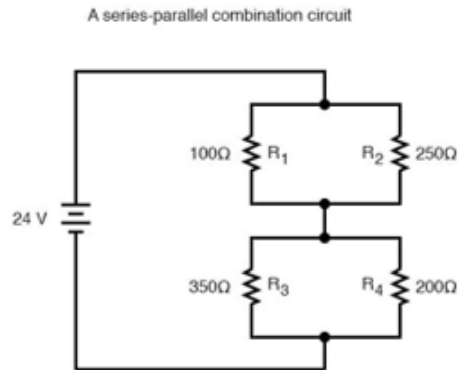
- Shares elements of both series and parallel circuit configurations
- Allows for complex circuit designs to optimize performance & functionality



13

Notes:

- A **series-parallel circuit** is a combination of both series and parallel connections within the same circuit.
- Some components are arranged in a single path, while others have multiple pathways for current to flow.
- When examining a series-parallel circuit, it helps to look at one section at a time. Identify which portions act as a series circuit, and which parts act like parallel circuits. Then apply the same rules.
- If a component fails, it depends on where the failure occurred.
- A failure in a series section can stop current to all components downstream. However, a failure in a parallel branch may only affect that path; the rest of the circuit may continue to allow current to flow.

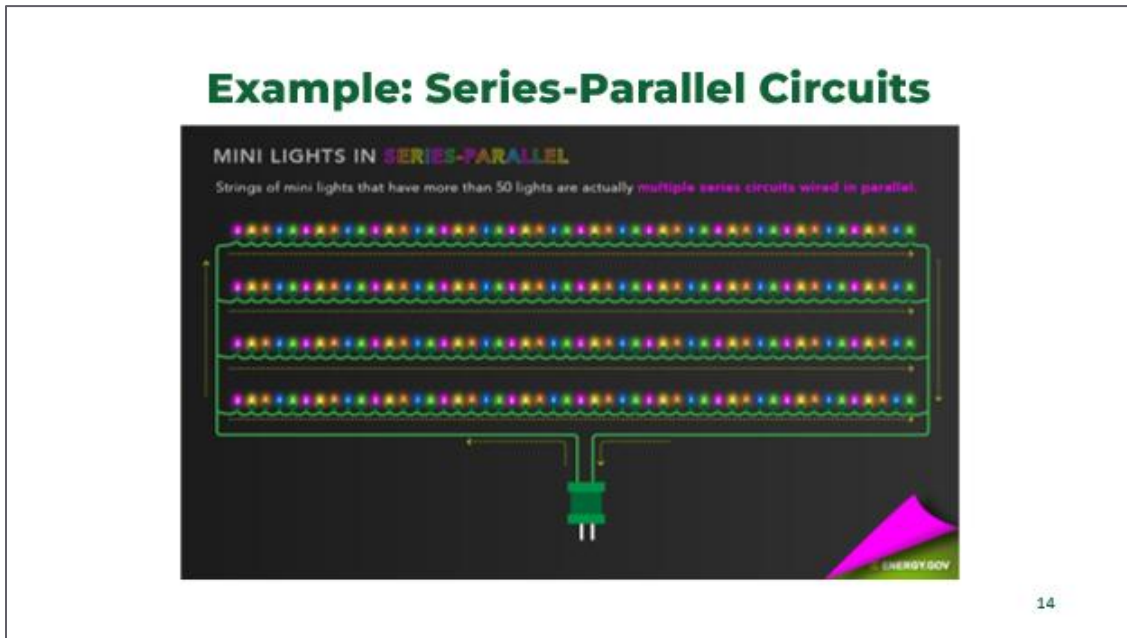


Notes:

- The slide shows a real-world example of a **series-parallel circuit** using holiday or mini lights.
- Each individual section of lights is wired **in series** — meaning within that small section, current flows through each bulb one after another.
- Then, those series sections are connected **in parallel** to each other.
- So, what does that mean functionally?
 - Within each small section (series), **voltage** is divided across the bulbs.
 - Across the larger branches (parallel), each section receives the same source **voltage**.
 - **Current** divides between the parallel branches.
- This design balances efficiency and reliability. If one entire series section fails, the other parallel branches can still operate.
- However, within a single series section, if one bulb opens (depending on the design) it may affect that entire section.


Instructor Demo: Circuit Configurations

SERIES

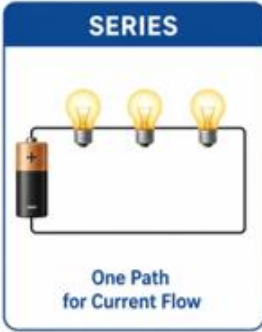


One Path
for Current Flow

PARALLEL

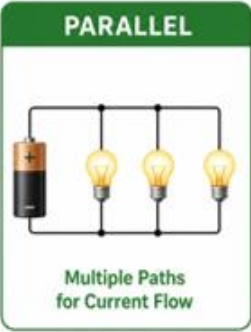

Multiple Paths
for Current Flow

SERIES-PARALLEL

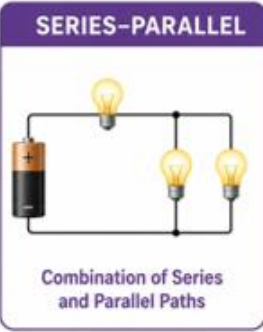

Combination of Series
and Parallel Paths

Observe: Bulb Brightness | Current Paths | Effect of Removing a Bulb

15

Notes:

- Watch your instructor demonstrate how to configuration each of the type of circuits.
- Series Circuit
 - What do you think will happen when power is applied?
 - What happens if one bulb is removed?
 - Remember: **In a series circuit, current has only one path. If any component opens, the entire circuit stops working.**
- Parallel Circuit
 - How do you think this circuit will behave differently?
 - What happens when one bulb is removed?
 - Remember: **Parallel circuits provide multiple current paths. A failure in one branch does not stop current flow through the others.**
- Series-Parallel
 - Would you classify this circuit as series or parallel?
 - What do you think happens when one bulb is removed?
 - Remember: **Series-parallel circuits combine characteristics of both circuit types. The effect of a failure depends on where the component is located within the circuit.**
- Now after the full demonstration, discuss with your instructor the following debrief questions:

Module 4 – Circuit Components & Architecture

- Which circuit provided only one path for current flow?
- Which circuit continued operating after a bulb was removed?
- Why are parallel circuits commonly used in electrical systems?
- How might these circuit configurations appear in transit vehicles and facilities?

Finally, one key takeaway:

Series circuits have one path, parallel circuits have multiple paths, and series-parallel circuits combine both. Understanding these configurations helps technicians troubleshoot electrical systems more effectively.

Activity: Drawing Circuits



Part I – Drawing Circuits

Use the symbols to draw a series circuit diagram and a parallel circuit diagram. Be sure to include **all** of the components in the chart below in your diagram.

Part II – Scenario Analysis

Read the “Simple Series Circuit Failure” scenario to **(1)** identify the failed component and **(2)** where the failure occurred in the circuit. Next, draw the circuit and label the failure.

Activity

Drawing Circuits

Part I – Drawing Circuits
Use the symbols below to draw a series circuit diagram and a parallel circuit diagram. Be sure to include all of the components in the chart below in your diagram.

SYMBOL	NAME	UNIT	SYMBOL
	RESISTOR	Ω	
	VARIABLE RESISTOR	Ω	
	CAPACITOR	F	
	INDUCTOR	H	

1. Draw a series circuit diagram in the space below.

2. Draw a parallel circuit diagram in the space below.

© 2026 Transit Workforce Center - Pg. 1

Activity: Drawing Circuits

Scenario – Simple Series Circuit Failure

A technician is troubleshooting a small 12V lighting circuit on a vehicle. The circuit includes a battery, a switch, and three lights wired in series.

When the switch is turned on, none of the lights illuminate. The battery has been tested and is good. The switch is confirmed to be closed and functioning properly.

After inspecting the lights, the technician finds that one bulb has a broken filament.



17

Notes:

Helpful information:

- Series circuits are useful in alarm circuits because any break or open in the circuit stops current flow and triggers an alarm condition. In these systems, the loss of power or current is what signals the problem.
- Parallel circuits are useful when multiple devices need to operate from one power source. Because current has multiple paths to flow, one device can fail while the others continue operating. This is common in house wiring and other systems where you do not want one failed load to shut down the entire circuit.
- Series-parallel circuits combine features of both series and parallel circuits. These are very common in bus, shop, and signal systems because they allow electrical systems to be designed for different operating needs.







Activity

Drawing Circuits

Part I – Drawing Circuits

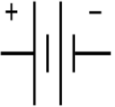Use the symbols below to draw a series circuit diagram and a parallel circuit diagram. Be sure to include all of the components in the chart below in your diagram.

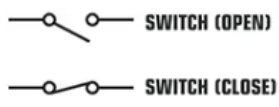Electric potential source or battery	Load	Fuse	Switch(es)
			

1. Draw a **series circuit diagram** in the space below.

2. Draw a **parallel circuit diagram** in the space below.

Part II – Scenario Analysis


Read the “Simple Series Circuit Failure” scenario to **(1)** identify the failed component and **(2)** where the failure occurred in the circuit. Next, draw the circuit and label the failure.

Simple Series Circuit Failure

A technician is troubleshooting a small 12V lighting circuit on a vehicle. The circuit includes a battery, a switch, and three lights wired in series.

When the switch is turned on, none of the lights illuminate. The battery has been tested and is good. The switch is confirmed to be closed and functioning properly.



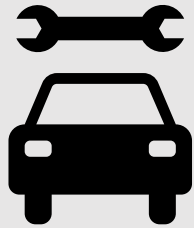
After inspecting the lights, the technician finds that one bulb has a broken filament.



Knowledge Check

Identify and describe the function of each type of circuit below.

1.

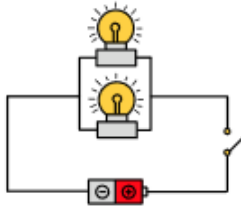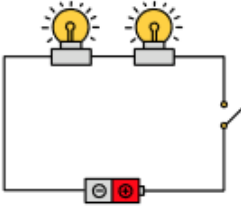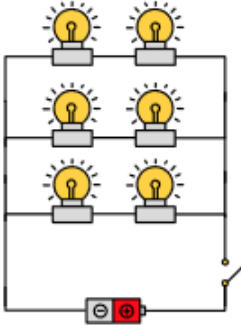

18

Notes:

Helpful information:

- Series circuits are useful in alarm circuits because any break or open in the circuit stops current flow and triggers an alarm condition. In these systems, the loss of power or current is what signals the problem.
- Parallel circuits are useful when multiple devices need to operate from one power source. Because current has multiple paths to flow, one device can fail while the others continue operating. This is common in house wiring and other systems where you do not want one failed load to shut down the entire circuit.
- Series-parallel circuits combine features of both series and parallel circuits. These are very common in bus, shop, and signal systems because they allow electrical systems to be designed for different operating needs.

Summary and What's Next


- ✓ Electrical Circuits are closed paths that allow electrons to flow.
- ✓ Open vs. closed circuits determine whether electricity can flow.
- ✓ Series circuits have one path for current.
- ✓ Parallel circuits have multiple paths for current.
- ✓ Series-parallel circuits combine both types.

Next, we'll continue our exploration of current and voltage by learning how Kirchoff's Laws helps technicians analyze electrical circuits.

19


Notes:

- An electrical circuit is a **closed path** that allows electrons to flow.
 - Whether a circuit is **open or closed** determines if current can move through the system.
 - We discussed how **series circuits** have only one path for current — meaning one break stops everything.
 - We also covered **parallel circuits**, which provide multiple paths — so one branch can fail without shutting down the entire system.
 - And finally, we looked at **series-parallel circuits**, which combine both configurations. These are common in real-world systems, especially in transportation and facility electrical systems.
 - Before we move on...
 - In a series circuit, what happens if one component fails?
 - In a parallel circuit, what electrical value stays the same across each branch?
 - **The key takeaway:** Understanding circuit architecture helps you predict how a system will behave — and how it will fail.
 - **Next , we'll continue our exploration of current and voltage by discussing Kirchoff's Laws. Then, we'll review the components that move, control, and power a circuit.**
-
-
-
-
-

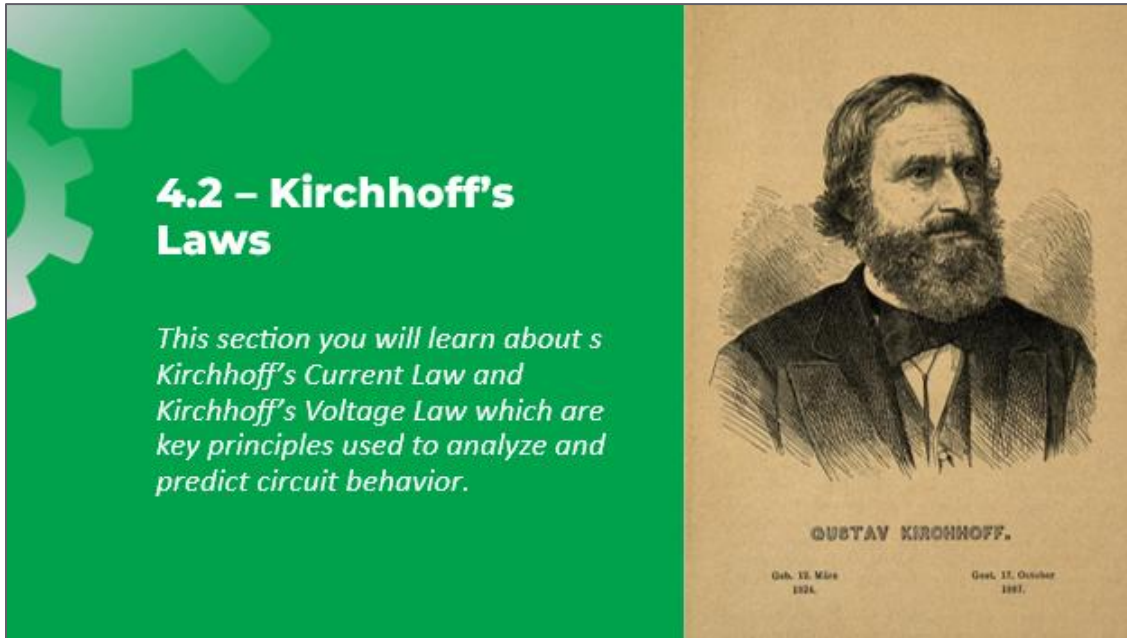

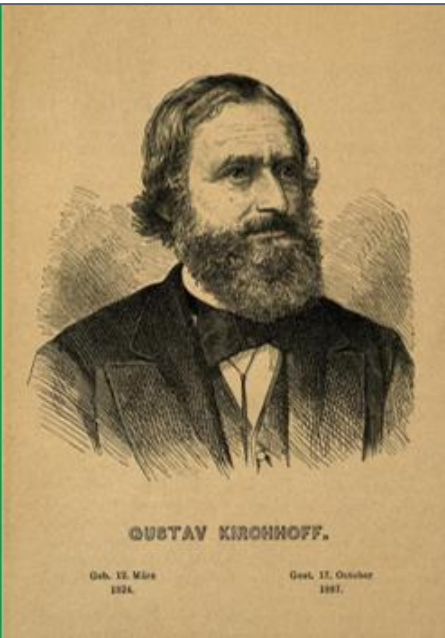4.2 – Kirchhoff's Laws

This section you will learn about s Kirchhoff's Current Law and Kirchhoff's Voltage Law which are key principles used to analyze and predict circuit behavior.



GUSTAV KIRCHHOFF.

Geb. 12. März 1824. Gest. 17. October 1887.


Notes:

- This section you will learn about Kirchhoff's Current Law and Kirchhoff's Voltage Law which are key principles used to analyze and predict circuit behavior.

Kirchhoff's Laws: The Rules for the Whole Circuit

Ohm's Law
Relationship between voltage, current, and resistance in a *single part* of a circuit

Kirchhoff's Laws
Explains how current and voltage behave across the *entire circuit*







The diagram features a magnifying glass on the left, focusing on a circuit diagram with a motor, a resistor, and a light bulb. On the right, there are stylized gears in green and yellow, with the number '21' positioned below them.

Notes:

- You've learned that **Ohm's Law** explains the relationship between voltage, current, and resistance in a *single* part of a circuit.
- Think of Ohm's Law *like zooming in* with a magnifying glass. We're looking at **one** resistor, one light, one motor, etc.
- **Kirchhoff's Laws** *zoom back out*. They explain how current and voltage behave across the **entire circuit** — how everything connects and stays balanced.
- Without Kirchhoff's Laws, we can't analyze complex circuits, especially series-parallel systems.
- So now it's shifting from component-level thinking to system-level thinking.

Kirchhoff's Laws On the Job

You use Kirchhoff's Laws every time you:

-  • Check voltage drop across multiple components
-  • Diagnose dim lights or weak motors in a series circuit
-  • Look for shorts or broken wires
-  • Confirm system balance after a repair



Notes:


- Kirchhoff's Laws are important because it isn't just theory. This is exactly what you do when you troubleshoot.
- You use Kirchhoff's Laws any time you:
 - Check voltage drop across multiple components
 - Diagnose dim lights or weak motors in a series circuit
 - Look for shorts or open connections
 - Confirm the system is balanced after a repair
- You might not call it "Kirchhoff's Law" at work — but when you expect voltage to add up or current to split correctly, that's Kirchhoff.
- If voltage or current doesn't balance, something is open, shorted, loose, or corroded. That imbalance is your diagnostic clue.

Kirchhoff's Current Laws (KCL)

KCL: The current **going into a junction** is equal to the current **coming out**.

Formula: $I_{in} = I_{out}$

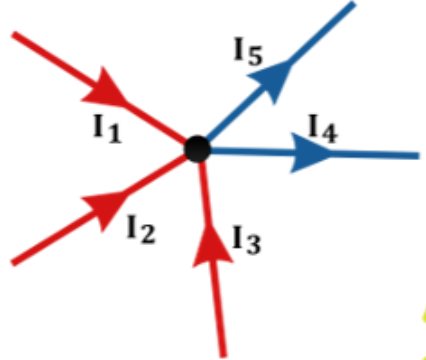A **junction** is where two or more branches meet, allowing current to divide or rejoin



$I_1 + I_2 + I_3 = I_4 + I_5$

23

Notes:

- Kirchhoff's Laws help us understand how current and voltage behave in electrical circuits, especially when things get more complex with multiple branches or loops.
- **Kirchhoff's Current Law**, referred to as **KCL** for short, states that the current going into a **node** (or **junction**) is equal to the current coming out.
 - In other words, current flowing *into* the circuit is equal to the current flowing *out of* the circuit.
- A **junction** is a point in an electrical circuit where two or more conductors or branches meet, allowing current to split into different paths or combine back together.
 - Think of it like traffic at an intersection- what goes in must come out.
- All the current flowing into that junction point must flow out through the available paths.
 - Current doesn't pile up or disappear at a junction; it splits up depending on the load and circuit design.
- That junction is also where different paths can lead into separate loops, and each of those loops still follows Kirchhoff's Voltage Law.
- Even though the current divides at the junction, the voltage remains constant at these junctions. Circuits design may also be a factor.

Application: Kirchhoff's Current Laws

KCL: The current **going into** a **junction** is equal to the current **coming out**.

Example:
 $I_1 + I_2 + I_3 = I_4 + I_5$


The diagram shows a central junction point where five wires meet. Three red arrows, labeled I_1 , I_2 , and I_3 , point towards the junction. Two blue arrows, labeled I_4 and I_5 , point away from the junction. A black box above the junction contains the text "Total = 6A". A yellow box with a question mark is next to the I_5 arrow. Labels "2a" are placed near the red arrows, and "3a" is near the I_4 arrow. In the bottom right corner, there are green gears and the number "24".

Notes:

- Remember, KCL tells us that the total current entering a junction equals the total current leaving. What goes in must come out!
- This is especially helpful when analyzing complex circuits—instead of trying to follow every path, you can focus on the junction and use KCL to find missing values.
- For example, if you have five wires meeting at a node and you know the current in four of them, you can calculate the fifth by making sure the total in equals the total out.
- Take a look at the example on the slide:
 - We know that the junction is **6A**.
 - That means the current **coming in** (red arrows) equals **6A**.
- According to KCL, the current **coming out** (blue arrows) also needs to equal **6A**. So, if I_4 is 3A, what does I_5 equal?
- We know this is correct because we have 6A coming in and 6A going out. Think of it like balancing the flow of traffic at an intersection.

Kirchhoff's Voltage Laws (KVL)

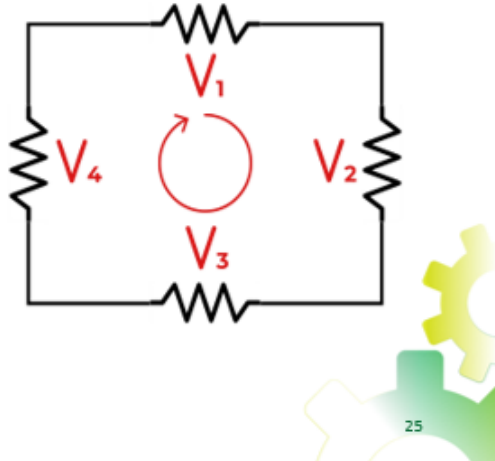- **KVL:** The sum of all voltages around a closed loop equals **zero**
- **Formula:**
$$+V_{source} - V_1 - V_2 - V_3... = 0$$
- All supplied voltage (V_{source}) is **used** within the loop ($V_1 - V_2 - V_3...$)



Notes:

- **Kirchhoff's Voltage Law**, referred to as KVL, states that the sum of all voltages around a closed loop equals **zero**. What that means practically is this:
 - Any voltage supplied by the source must be completely accounted for within the loop.
 - As current moves through the circuit, each component uses some voltage.
 - By the time you return to the source, all the voltage has been “used” or dropped across the components.
- You can think of this like an energy accounting system. Whatever energy the source provides must be fully spent across the resistors, lights, motors, or other loads in that loop.
- If the numbers don't add up, something is wrong. It could be a bad connection, incorrect measurement, or a hidden fault.
- Kirchhoff's Laws, both Voltage and Current, are foundational tools for analyzing and troubleshooting circuits, especially those with multiple loops or branches.
- Once you understand the logic, they become powerful diagnostic tools in real-world systems.


Additional Video: <https://www.youtube.com/watch?v=ZDoylghUI44>

Application: Kirchhoff's Voltage Laws

KVL: The sum of all voltages around a closed loop equals **zero**

Formula:
 $+V_{source} - V_1 - V_2 - V_3... = 0$

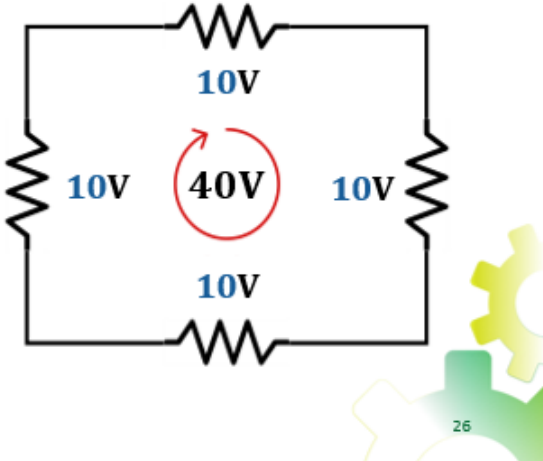Voltage Drop Example:
 $40V - 10V - 10V - 10V - 10V = 0$
 $0V = 0$



Notes:

- Again, Kirchhoff's Voltage Law tells us that the sum of all voltages around a closed loop must equal **zero**.
 - This principle is used to find unknown voltages in a circuit by making sure that all the voltage supplied is completely used up by the components in the loop—nothing extra, nothing missing.
 - For example, if you have a loop with one voltage source and several resistors, KVL allows you to calculate the voltage drop across each resistor. It's like making sure every dollar you spend adds up exactly to the amount of money you had at the start.
 - In any circuit, a **voltage drop across a component** represents the amount of voltage that component uses. (Remember voltage drops are considered negative voltage)
 - According to Kirchhoff's Voltage Law, the sum of all voltage drops in a closed loop must equal the source voltage — so when we add them algebraically around the loop, the total equals zero.
 - In this example, we have a 40-volt source and four resistors of equal resistance connected in series.
 - Because the resistors are equal, the voltage divides evenly across them.
 - If 40 volts is supplied to the circuit and there are four equal resistors, how much voltage will each resistor drop?
-
-
-
-
-

Part 1 and 2: Kirchhoff's Laws Practice Problems



Directions: Use Kirchhoff's Current and Voltage Laws to solve the equations below.

Part 1: Kirchhoff's Current Law

- Find the unknown current.

Part 2: Kirchhoff's Voltage Law

- Calculate the unknown voltage drop.

Please complete only Parts 1 and 2 for now.

Activity

Kirchhoff's Laws Practice Problems

Directions: Use Kirchhoff's Current and Voltage Laws to solve the equations below.

Kirchhoff's Current Law	Kirchhoff's Voltage Law
<p>The sum of all currents entering a node is equal to the sum of all currents leaving the node.</p> <p>Law: $\sum I_{in} = \sum I_{out}$</p>	<p>The sum of all voltage drops around a closed loop equals zero.</p> <p>Law: $\sum V_{drops} = \sum V_{sources} = 0$</p>
<p>Example:</p> <p> $I_1 + I_2 = I_3$ $2A + 1A = 3A$ $3A = 3A$ </p>	<p>Example:</p> <p> $\sum V_{drops} = \sum V_{sources} = 0$ $\sum V_{drops} = 10V + 10V + 10V = 0$ $30V = 0$ </p>

Part 1: Kirchhoff's Current Law

1. Find the unknown current. The first step of problem solving has been done for you.

$I_1 = I_2 + I_3$

2. Find the unknown current. The first step of problem solving has been done for you.



$I_1 = I_2 + I_3 + I_4$

© 2026 Transit Workforce Center - Pg. 1

Activity

Kirchhoff's Laws Practice Problems


Directions: Use Kirchhoff's Current and Voltage Laws to solve the equations below.

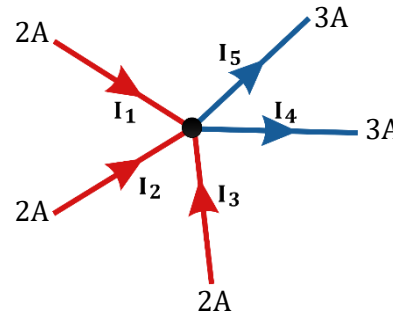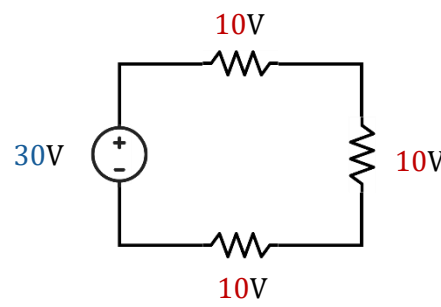Kirchhoff's Current Law	Kirchhoff's Voltage Law
The current going into a junction is equal to the current coming out. $I_{in} = I_{out}$	The sum of all voltages around a closed loop equals zero. $+V_{source} - V_1 - V_2 - V_3... = 0$
Example:  $I_1 + I_2 + I_3 = I_4 + I_5$ $2A + 2A + 2A = 3A + 3A$ $6A = 6A$	Example:  $+V_{source} - V_1 - V_2 - V_3 = 0$ $+V_{30} - V_{10} - V_{10} - V_{10} = 0$ $0 = 0$

Part 1: Kirchhoff's Current Law


- Find the unknown current. The first step of problem solving has been done for you.

$$I_1 + I_3 = I_2$$

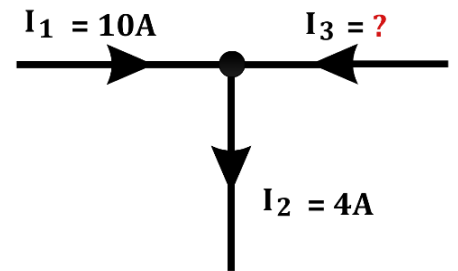


- Find the unknown current. The first step of problem solving has been done for you.


$$I_1 + I_3 = I_2 + I_4$$

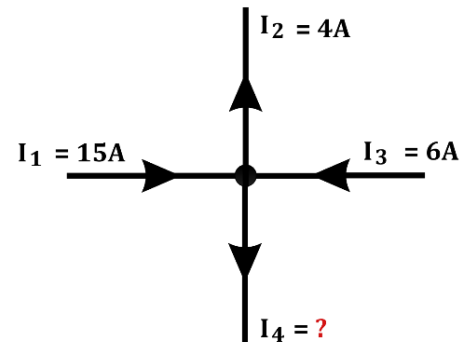


3. Find the unknown current.

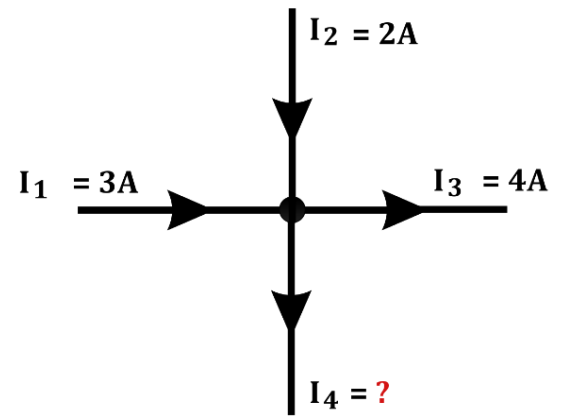

4. Find the unknown current.

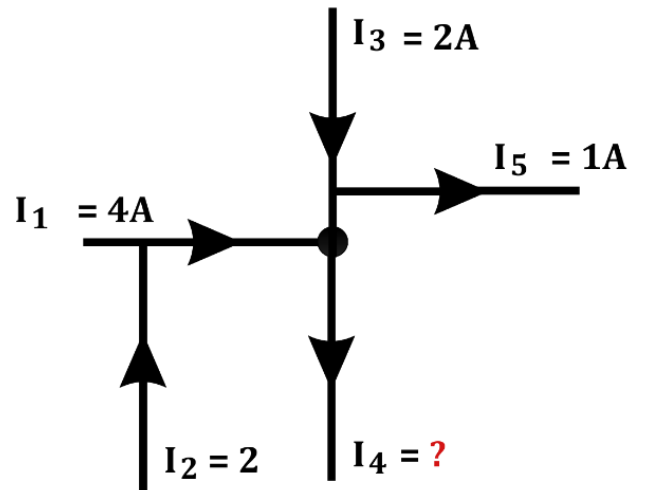


5. Find the unknown current.

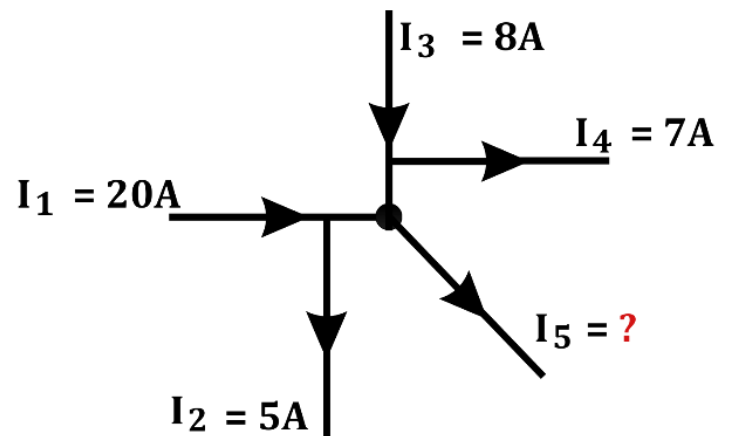


Part 2: Kirchhoff's Voltage Law

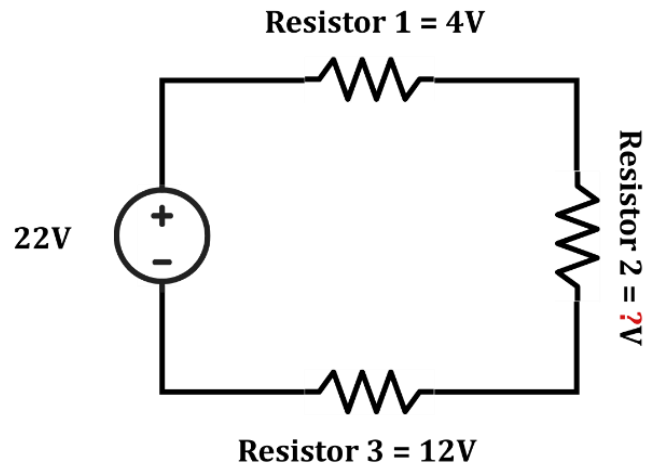
6. Calculate the unknown **voltage drop** across Resistor 2.



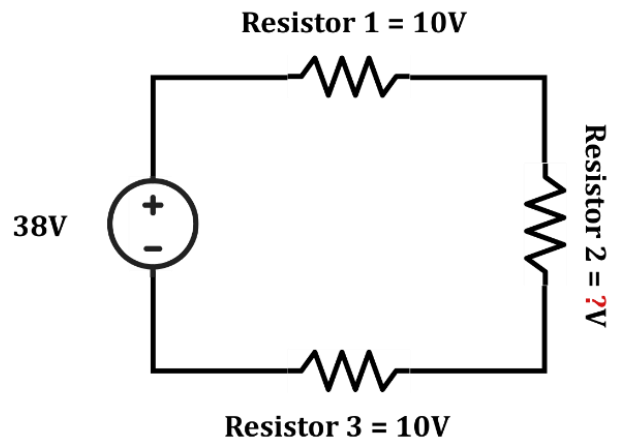-
7. Calculate the unknown **voltage drop** across Resistor 2.




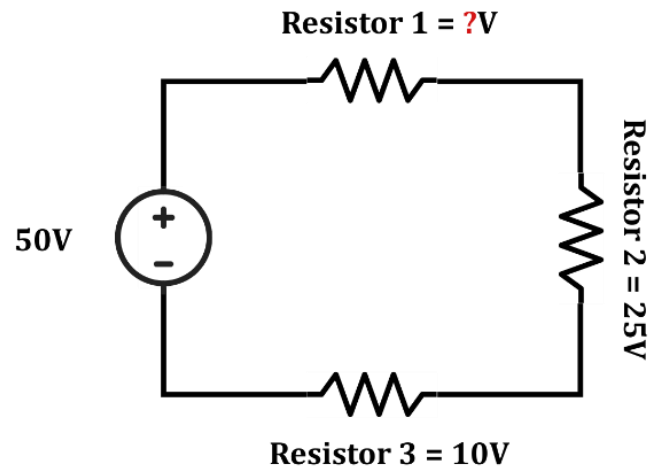-
8. Calculate the unknown **voltage drop** across Resistor 1.



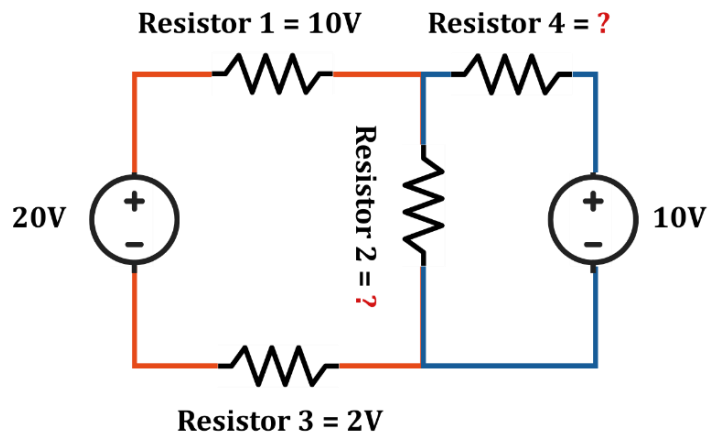
9. Calculate the unknown **voltage drop** across Resistor 2 and 4. First, calculate the voltage drop in the **orange** circuit. Next, solve the voltage drop in the **blue** circuit. The first step in the equation has been done for you.

$$+V_{\text{source}} - V_1 - V_2 - V_3 = 0$$



10. Calculate the unknown **voltage drop** across Resistor 2 and 4. First, calculate the voltage drop in the **orange** circuit. Next, solve the voltage drop in the **blue** circuit. The first step in the equation has been done for you.


$$+V_{\text{source}} - V_1 - V_2 - V_3 = 0$$

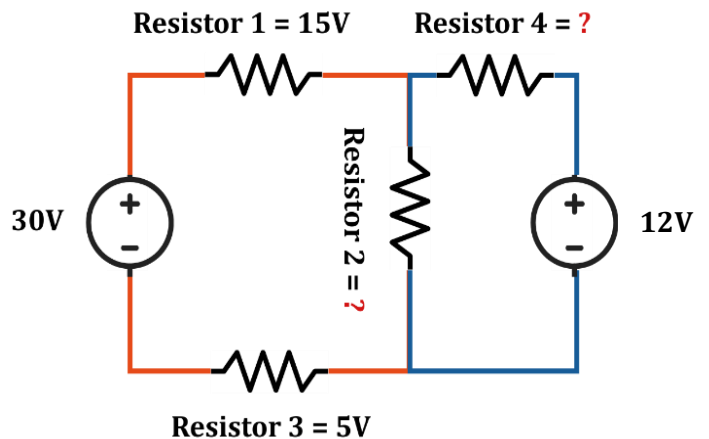


Part 3: Write Your Own Equations

- Using the diagrams below, write two practice problems using Kirchoff's Current Law and two practice problems using Kirchoff's Voltage Law.
- Give your paper to a partner and have them solve your equations.
- Get your paper back from your partner and check their work.

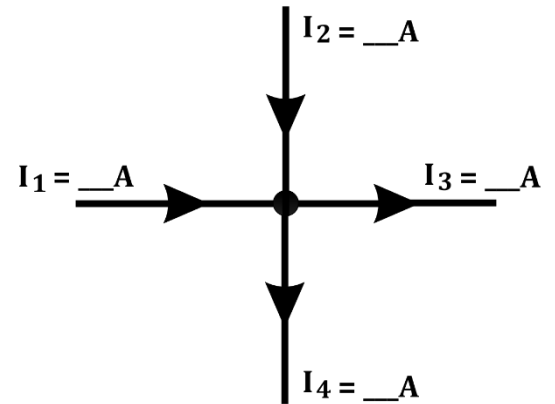
11. **KCL** Practice Problem - Find the **unknown current**.



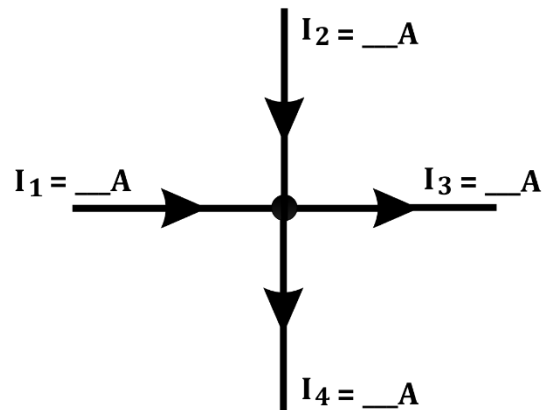
12. **KCL** Practice Problem - Find the .



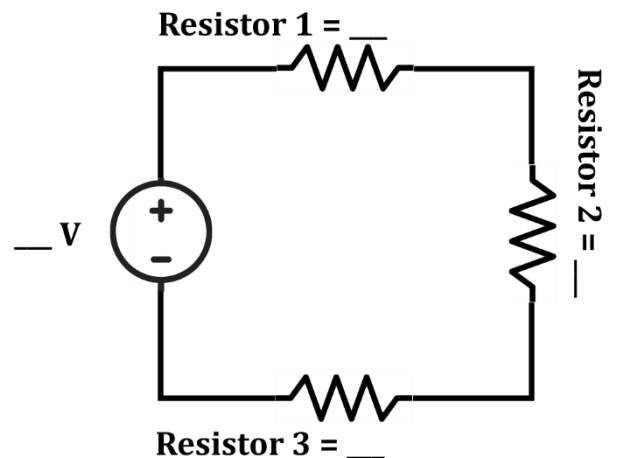13. **KVL** Practice Problem - Calculate the unknown **voltage drop**.



14. **KVL** Practice Problem - Calculate the unknown **voltage drop**.

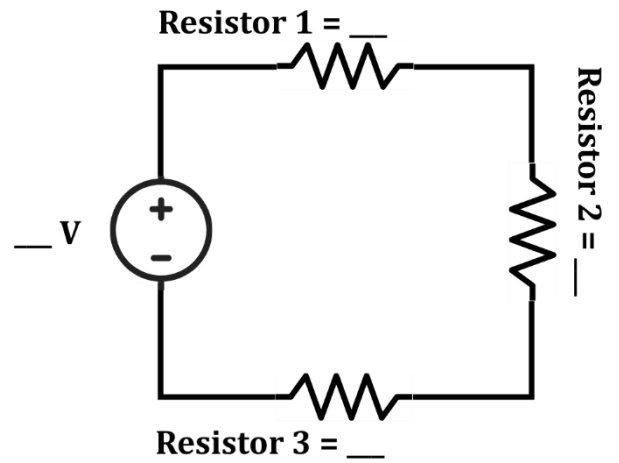

Question 1




1. Find the unknown current. The first step of problem solving has been done for you.

Solution:

$$I_1 + I_3 = I_2$$

Check:

$$I_1 + I_3 = I_2$$

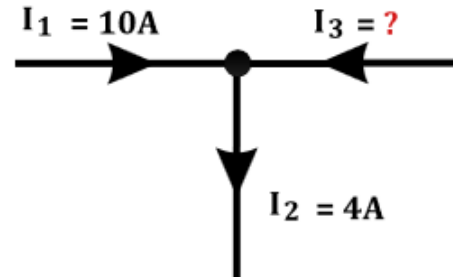

28

Question 6




6. Calculate the unknown **voltage drop** across Resistor 2.

Solution:

$$+V_{\text{source}} - V_1 - V_2 - V_3 = 0$$

Check:
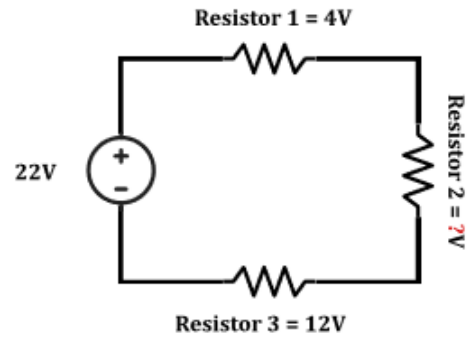
$$+V_{\text{source}} - V_1 - V_2 - V_3 = 0$$



29

Part 3: Kirchhoff's Laws Practice Problems

Part 3: Write Your Own Equations

- Using the diagrams, write two practice problems using **KCL** and two practice problems using **KVL**.
- Give your paper to a partner and have them solve your equations.
- Get your paper back from your partner and check their work.

Notes:

- Use the following questions to debrief:
 1. *Were you able to solve your partner's problems? If not, where did you make an error?*
 2. *What was the easiest part of this activity? What was the most challenging?*

Knowledge Check



According to Kirchhoff's Current Law, _____.

- A. The current going into a junction is equal to the current coming out.
- B. Voltage across a component equals the current flowing through it multiplied by its resistance.
- C. The sum of all voltages around a closed loop equals zero.
- D. The current will be removed from the circuit.

31

Knowledge Check



According to Kirchhoff's Voltage Law, the sum of all voltages around a closed loop in a circuit must be _____.

- A. Equal to the highest voltage in the loop
- B. Greater than the battery voltage
- C. Less than the sum of voltage drops
- D. Equal to zero

32




Notes:

- Next, we'll explore the main parts found inside an electrical circuit.

Wires

- Flexible cable that carries electrical current between components in a circuit



The diagram shows a cross-section of a cable. It features a blue outer jacket, a white protective sleeve, a red insulation layer, and several copper conductive strands. An arrow points to the white sleeve with the label 'Protective Sleeve'. In the bottom right corner of the diagram area, there is a small number '34' and some faint gear icons.

Notes:

- When we talk about wires, we need to discuss two terms we learned about in previous modules: **conductor** and **insulator**.
- A **wire** is a flexible cable that serves as the pathway to carry an electrical current and allows flow between components in a circuit.
- If you look at the image on the slide, it shows a common cable breakdown of several parts of an individual strand of wire.
- Wires can either act as either:
 - a **conductor** which allows electricity flow easily like metals like copper, aluminum, steel, and high-strength alloys.
 - or **insulator** which resists or blocks flow of electricity like rubber or plastic.
- If conductors carrying electrical current were not insulated and came into contact with the ground, the electricity would take an unintended path straight to the ground.
- This is because electricity always looks for the easiest path to return to its source, and the ground often provides a low-resistance route.

Wire Gauges Size & Wire Ampacity Table

WWW.ELECTRICTECHNOLOGY.ORG

 <p>3/0 Gauge</p>	<p>200 AMPS Service Entrance - From Utility Pole to Energy Meter</p>
 <p>1/0 Gauge</p>	<p>150 AMPS Service Entrance & Feeder Wire - To Panel Box</p>
 <p>3 Gauge</p>	<p>100 AMPS Service Entrance & Feeder Wire - To Panel Box</p>
 <p>6 Gauge</p>	<p>55 AMPS Feeder & Large Appliance Wire</p> 
 <p>8 Gauge</p>	<p>40 AMPS Feeder & Large Appliance Wire</p>
 <p>10 Gauge</p>	<p>30 AMPS Appliances e.g. Dryer, Air-conditioning, Water Heater</p>
 <p>12 Gauge</p>	<p>20 AMPS Appliances like Laundry, Bathroom & Kitchen Circuits</p>
 <p>14 Gauge</p>	<p>15 AMPS General Lighting, Fans & Outlet / Receptacle Circuits</p>

Wire Dimensions

- **Length** – Distance of wire from one end to the other
- **Diameter** – the cross-sectional width (or thickness) of a wire; typically measured in inches or millimeters
- **Gauge**– Size of a wire’s diameter

3/0 Gauge	200 AMPS Service Entrance - From Utility Pole to Energy Meter
1/0 Gauge	150 AMPS Service Entrance & Feeder Wire - To Panel/Box
3 Gauge	100 AMPS Service Entrance & Feeder Wire - To Panel/Box
6 Gauge	55 AMP Feeder & Large Appliances
8 Gauge	40 AMP Feeder & Large Appliances
10 Gauge	30 AMP Appliances e.g. Stoves, Dryers
12 Gauge	20 AMP Appliances like Dishwashers
14 Gauge	15 AMP General Lighting



35

Notes:

- **Wire length** is the distance of wire from one end to the other.
 - Electrical wire can come in rolls or on spools. Lengths of wire vary from standard cuts of 50, 100, 250, 500 and 1,000 feet, but can be special ordered for specific lengths.
- **Wire gauge** is the size of a wire’s diameter.
 - The size of wires affect the amount of electricity that can flow and how safely.
 - The smaller the number of the wire, the bigger the gauge will be.
- **Wire diameter** is the cross-sectional width (or thickness) of a wire and is typically measured in inches or millimeters.

Electrical (Power) Source

- Component that generates **electrical energy** and pushes it through a circuit
- Creates the **voltage** that drives current flow
- Voltage = Difference in electrical charge between two points
- Examples: batteries, solar panels, generators, substations



Notes:

- A **power source** is the component that generates electrical energy and pushes it through a circuit.
 - More specifically, electric current consists of free electrons moving through a conductor.
 - As those electrons move from atom to atom, they transfer energy through the circuit.
- So, what does a power source actually do?
 - It creates **voltage** — the electrical pressure that drives current through the system.
- Voltage is the difference in electrical charge between two points. Without that difference in charge, electrons would not move.
- As we continue through this module, you'll see that voltage works together with two other key elements: **current and resistance**. Those relationships are critical to understanding circuit behavior.
- **Common power sources include:**
 - a) Batteries (AA, coin cells, solar storage batteries)
 - b) Solar panels, which convert sunlight into electrical energy
 - c) Generators, often used as backup power
 - d) Electrical substations, which distribute power across larger systems
- Every circuit must have a source — without it, there is no energy to move.

Load

- Component or device that consumes energy in circuit
- Converts energy into a functional form or task (heat, light, motion, etc.)
- Example: Lightbulbs, motors, resistors, TVs, air conditioners, kitchen appliances, etc.



37

Notes:

- A **load** is any component within a circuit that uses electricity to carry out work.
- In other words, a load converts energy into a functional form or task, like producing heat, light or movement (motion).
- Besides the examples shown here on the slide, can you think of any additional examples?
- Examples include: lightbulbs (incandescent, LED), motors and traction motors, resistors, TVs, air conditioners & fans, kitchen appliances, etc.

Circuit Protection

- Safeguards built into a circuit to prevent electrical faults such as
 - Overcurrent
 - Short Circuit
 - Overvoltage
 - Ground Fault
- Prevents equipment damage, fires, and system failures
- Ensures system safety, reliability, and longevity



38

Notes:

- **Circuit protection** refers to the safeguards built into an electrical system to detect and prevent faults.
- Faults include things like:
 - a) **Overcurrent** occurs when current exceeds the rated limit of the circuit. This can overheat wires and components.
 - b) A **short circuit** happens when current finds an unintended low-resistance path — often bypassing the load. This can cause a rapid surge in current.
 - c) **Overvoltage** is a voltage spike that exceeds the system’s design limits. This can damage sensitive electronics.
 - d) A **ground fault** occurs when current unintentionally flows to ground, often due to damaged insulation or wiring.
- Electrical systems are designed to operate within specific limits. When those limits are exceeded, damage can occur — sometimes very quickly.
- Circuit protection helps prevent: Equipment damage, fires, system failures, safety hazards
- It also improves system reliability and extends the life of components.

Circuit Protection – s

- One-time devices designed to interrupt current when it exceeds a safe level
 - **Advantages:** Simple, low cost, reliable
 - **Disadvantages:** One-time use, must replace after blowing
- Types: Blade, Cartridge, High-Speed



39

Notes:

- A **fuse** is a one-time safety device that breaks the circuit when the current exceeds a safe level making it a simple and effective way to protect equipment.
- There are several types of fuses used in DC circuits, including:
 - a) Blade fuses – commonly found in automotive systems.
 - b) Cartridge fuses – used in a variety of industrial and residential settings.
 - c) High-speed fuses – designed to protect sensitive electronic components by reacting quickly to overcurrent.
- Some of the advantages of using fuses are that they're simple, low-cost, and reliable.
- They also help protect with electrical damage, short circuiting, voltage, overcurrent and blow outs, reducing fire hazards/risk, wire degradation.
- A main drawback is that once a fuse blows, it has to be replaced, as it's designed for one-time use only.

Circuit Protection – Circuit Breakers

- Reusable devices that interrupt current when it exceeds a safe level
 - **Advantages:** Reusable, easy reset, reliable
 - **Disadvantages:** Higher cost (compared to fuses)
- Types: Thermal, Magnetic, Hybrid



40

Notes:

- **Circuit breakers** are devices that interrupt current when it surpasses a level that is safe. Like fuses, circuit breakers offer protection against overcurrent.
- However, unlike fuses, circuit breakers are reusable devices that stop the flow of electricity when the current exceeds safe limits—they can be reset rather than replaced.
- Some key advantages of circuit breakers are that they're reusable, easy to reset, and very reliable.
- The main disadvantage is cost—they tend to be more expensive than fuses up front.
- In DC systems, common types of circuit breakers include:
 - a) Thermal breakers – which trip when heat from excessive current builds up.
 - b) Magnetic breakers – which use a magnetic field to quickly interrupt current during a surge.
 - c) Hybrid (thermal-magnetic) breakers – combine both mechanisms for more effective protection.

Knowledge Check



Which of the following describes what wire gauge is?

- A. A flexible cable that serves as the pathway to carry electrical current
- B. Distance of the wire from one end to the other
- C. Cross-sections width (thickness) of the wire
- D. The size of a wire's diameter



41

Knowledge Check




What is the main advantage of a circuit breaker over a ?



42

Switches

- A device that completes or breaks a circuit by preventing or allowing electrical current flow to a component
- When switch is “on” or “closed” this **completes** a circuit and allows current flow
- When switch is “open” or “off”, the circuit is **broken** and no current flows




43

Notes:

- A **switch** is a device that completes or breaks a circuit by preventing or allowing electrical current flow to a component.
 - When a switch is “on” or “closed” this completes a circuit and allows current flow.
 - When a switch is “open” or “off”, the circuit is broken which stops the flow of current.
- A switch gives us control over electricity, allowing current to flow only when it’s needed and stopping it when it is not needed.
- Some of the key switches shown in the picture are: Toggle, Push button, Rotary, etc.
- Do you know any other examples of switches?

Relays

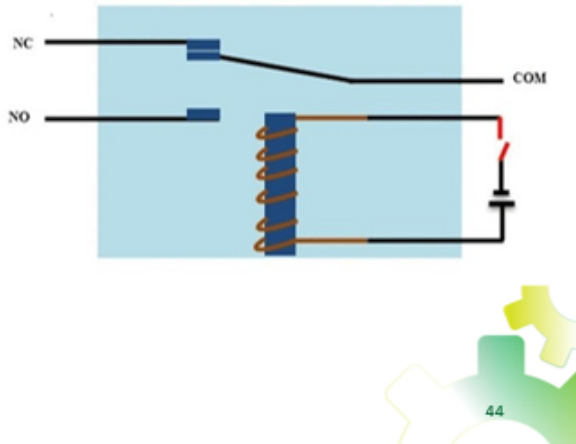- An electrical switch operated by an electromagnet
- Can allow low-power circuits to control high-power circuits
- Current flows through a coil generating a magnetic field that moves the switch to open or close



The diagram illustrates the internal components of a relay. It features a central blue rectangular electromagnet coil. To the left of the coil are two switch contacts: the top one is labeled 'NC' (Normally Closed) and the bottom one is labeled 'NO' (Normally Open). A common contact labeled 'COM' is positioned to the right of the coil. Wires connect these contacts to external terminals. A battery symbol is shown on the right side of the coil, indicating the power source for the electromagnet. The entire relay assembly is set against a light blue background. In the bottom right corner of the diagram area, there is a decorative graphic of interlocking gears in green and yellow, with the number '44' printed below them.

Notes:

- A **relay** is an electromechanical switch operated by an electromagnet, which can allow low-power circuits to control high-power circuits.
- As current flows through a coil it generates magnetic field, and if it moves through a switch it opens or closes the circuit.
- Applications of relays include:
 - Controlling high-current devices (motors, lights, heating elements).
 - Isolating low-power control systems from high-power circuits (for safety).
 - Automotive systems, industrial machinery, home appliances.
- In transit, you may see an electromagnet at work when doors in a bus open. To open the doors, an electrical signal is sent to a relay, which in turn sends electrical current to activate lights in the stepwell to provide better illumination.
 - When the doors close, the signal is interrupted, which then extinguishes the step lights. This is done automatically without driver intervention.

Relays: Normal Open vs Normal Closed

These terms refer to a relay's contact(s) default state when no power is being applied (Normal = De-energized)

Normal Open (NO)

- Contact open; When energized, contact closes & current **flows**



Normal Closed (NC)


- Contact closed; When energized, contact opens & current stops



45

Notes:

- Relay contact positions: The terms Normally Open (NO) and Normally Closed (NC) refer to the default state of a relay's contacts when **no power** is applied to the coil.
 - "Normal" simply means the relay is **de-energized**.
- When the relay's coil becomes energized, the contacts **switch** from their normal state to the opposite state. That switching action allows connected circuits to open or close. So, a relay is essentially an electrically controlled switch.
- A **Normally Open** contact does **not** allow current to flow when the relay is at rest. When the coil is energized, the contact closes and allows current to pass.
 - Think of it like a push-button light switch that only works while you are pressing it.
 - No power to the coil → circuit open.
Power applied → circuit closes.
- A **Normally Closed** contact allows current to flow when the relay is at rest. When the coil is energized, the contact opens and interrupts current flow. A good example is a refrigerator light switch.
 - The light is on by default. When the door closes (activating the switch), the circuit opens and the light turns off.
 - You'll also see this logic used in emergency alarm circuits
- Some relays control *more than one* circuit at the same time.
- A **double-pole** relay controls two separate circuits independently.
- A **triple-pole** relay controls three separate circuits.
- Each circuit has its own set of contacts, but all are controlled by the same coil. This allows one control signal to switch multiple circuits simultaneously.

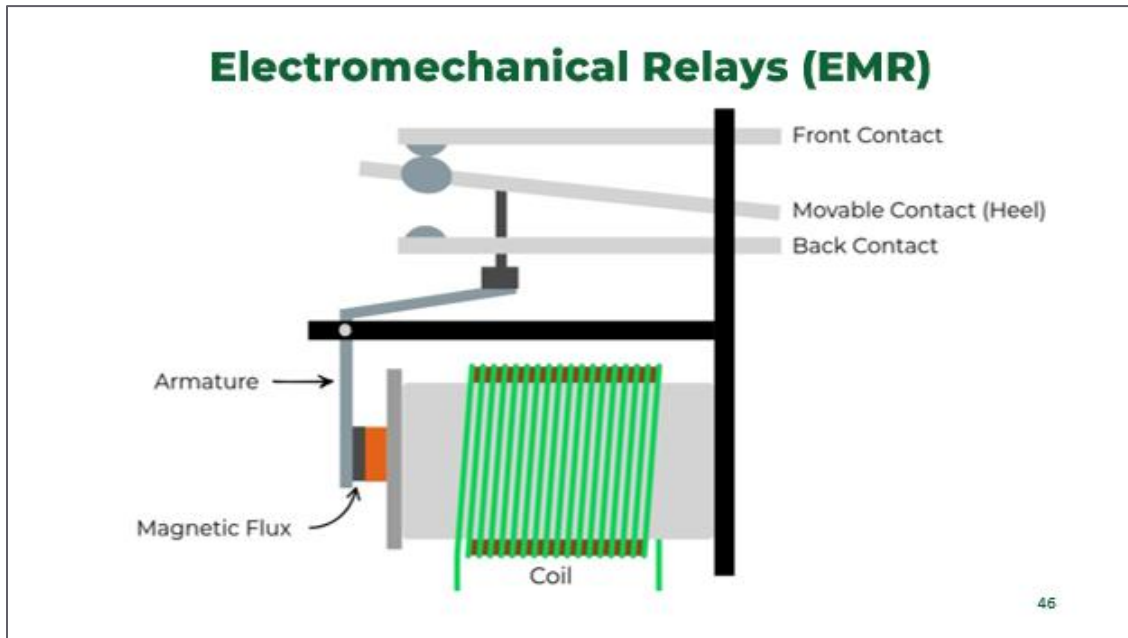

Notes:

- There are several kinds of relays.
- On the slide is a standard type Electromechanical Relays (EMRs) which uses physical moving contacts and a coil to switch circuits.
- Applications for EMRs include industrial machines, automotive systems, appliances.

Resistors

- A passive electric component that converts electrical energy into heat to control and limit current flow
- **Resistance** measured in ohms (Ω)
- **Power Rating** – maximum power the resistor can dissipate safely (measured in watts)
- **Tolerance** – indicates how close resistance value is to its stated value (e.g. $\pm 5\%$)



Notes:

- A **resistor** is a basic, passive component with two terminals. It is designed to help control the flow of current by providing resistance.
- This helps protect components, manage voltage drops, and helps to keep equipment operating smoothly.
- It works by converting electrical energy into heat, which helps limit and control the flow of current.
- Resistors are essential for:
 - Controlling current levels
 - Adjusting signal strength
 - Safely ending (terminating) transmission lines
- A few key terms to know:
 - **Resistance** (R) is measured in ohms (Ω)—it tells us how much the resistor resists current.
 - **Power rating** is how much power (in watts) the resistor can handle without overheating.
 - **Tolerance** tells us how close the actual resistance value is to what's printed on the label—like plus or minus (\pm) 5%.

Types of Resistors

- **Fixed resistors** – have a set or constant resistance value
 - Carbon film, Metal film, Wire wound
- **Variable resistors** – allow adjustment of resistance
 - Potentiometers, Rheostats



48

Notes:

- Two common types of resistors are fixed resistors and variable resistors.
- **Fixed resistors** have a set or constant resistance value that does not change during normal operation.
 - They are used when a circuit needs a consistent, predictable amount of resistance to control current.
 - Types include carbon film, metal film, wire wound.
- **Variable resistors** will come with multiple terminals (or sliding terminals) and will allow for the resistance to be adjusted in the electrical circuit.
 - They are commonly used to fine-tune circuit behavior.
 - Types include potentiometers, rheostats.

Applications of Resistors

- Limit current in circuits to protect components
- Voltage division in power supply circuits
- Signal conditioning in audio & communication systems



49

Notes:


- Applications of Resistors can include:
 - Limiting current in circuits to protect components
 - Voltage division in power supply circuits
 - Signal conditioning in audio & communication systems



Resource

Resistor Color Code Chart

6 - Band

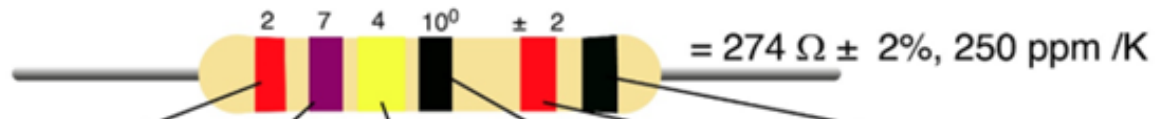


Color
Black
Brown
Red
Orange
Yellow
Green
Blue
Violet
Grey
White
Gold
Silver

1 st Digit	2 nd Digit	3 rd Digit
0	0	0
1	1	1
2	2	2
3	3	3
4	4	4
5	5	5
6	6	6
7	7	7
8	8	8
9	9	9

Multiplier
1 Ω
10 Ω
100 Ω
1k Ω
10k Ω
100k Ω
1M Ω
0.1 Ω
0.01 Ω

Tolerance
± 1 %
± 2 %
± 0.5 %
± 0.25 %
± 0.1 %
± 5 %
± 10 %

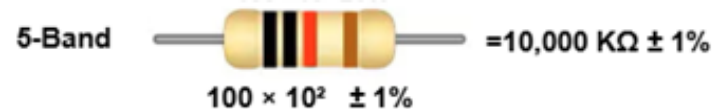Temperature Coefficient
250 ppm/K
100 ppm/K
50 ppm/K
15 ppm/K
25 ppm/K
20 ppm/K
10 ppm/K
5 ppm/K
1ppm/K



Resistor Color Codes

A standardized method for representing resistor values using colored bands.

- Bands 2-3: **digits**
- Next band is a **multiplier**
- Final band: **tolerance**
 - Gold = $\pm 5\%$,
 - Silver = $\pm 10\%$
 - None = $\pm 20\%$

Note Start reading from the side where the bands are closest to the edge and grouped together.

Color	1 st Digit	2 nd Digit	3 rd Digit	Multiplier	Tolerance	Temperature Coefficient
Black	0	0	0	1 Ω		250 ppm/K
Brown	1	1	1	10 Ω	$\pm 1\%$	100 ppm/K
Red	2	2	2	100 Ω	$\pm 2\%$	50 ppm/K
Orange	3	3	3	1k Ω		15 ppm/K
Yellow	4	4	4	10k Ω		25 ppm/K
Green	5	5	5	100k Ω	$\pm 0.5\%$	20 ppm/K
Blue	6	6	6	1M Ω	$\pm 0.25\%$	10 ppm/K
Violet	7	7	7		$\pm 0.1\%$	5 ppm/K
Grey	8	8	8			1 ppm/K
White	9	9	9			
Gold				0.1 Ω	$\pm 5\%$	
Silver				0.01 Ω	$\pm 10\%$	

50

Notes:


- **Resistor color codes** are a standardized way to label resistor values without printing numbers.
- Instead, resistors use colored bands to show their resistance and tolerance.
- Each color stands for a number — starting with black for 0, brown for 1, all the way up to white for 9.
- Most resistors have four or five bands.
 - The first two or three bands give you the digits, the next band is a multiplier, and the final band tells you the tolerance, or how much the actual resistance might vary from the stated value.
- For tolerance:
 - Gold means $\pm 5\%$
 - Silver means $\pm 10\%$
 - If there's no tolerance band, that means $\pm 20\%$
- So, how do you know which side to start reading from? Start reading from the side where the bands are closest to the edge and grouped together.

Resistors – Color Codes

How to Decode Resistor Color Bands

1. Identify the bands: 4-band, 5-band or 6-band configurations
2. Map colors to values: Use standardized color chart to identify digits, multipliers and tolerance

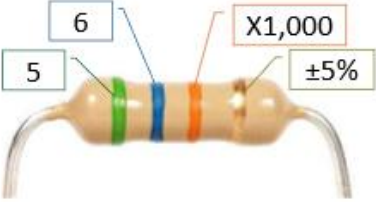Example:
Green = 5 (1st digit)
Blue = 6 (2nd digit)
Orange = $\times 1,000$ (multiplier)
Gold = $\pm 5\%$ (tolerance)
 $(5 \times 10 + 6) \times 1,000 = 56,000$ ohms (or 56 k Ω)



Note Start reading from the side where the bands are closest to the edge and grouped together.

51

Notes:


- To decode a resistor color band, first identify the band configuration.
- Next, map colors to values using the standardized color chart to identify digits, multipliers and tolerance.
 - Green = 5 (1st digit)
 - Blue = 6 (2nd digit)
 - Orange = $\times 1,000$ (multiplier)
 - Gold = $\pm 5\%$ (tolerance)
 - $(5 \times 10 + 6) \times 1,000 = 56,000$ ohms (or 56 k Ω)

Whole Class Practice

How to Decode Resistor Color Bands

1. Is this a 4, 5, or 6 band configuration?
2. What values will each color receive?

Example:

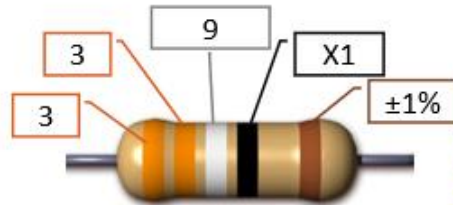

Note Start reading from the side where the bands are closest to the edge and grouped together.

52

Notes:

- Let's decode this resistor to determine the resistance.
 1. First, identify the bands. Is this a 4, 5, or 6 band configuration?
 2. Next, map the color values. What number will each color receive?
 3. So, what will the equation be?
 4. Calculating the final answer, which is:

Activity: Reading a Resistor




Part 1: In **small groups**, use the **resistors** provided by the instructor and the **Resistor Color Code Chart** to identify each resistor by reading its color bands. Use the space below to record the digits, multiplier, tolerance, and final resistance value.

Part 2: **On your own**, read each resistor and use the space provided to note the digits, multipliers, and tolerance.

The image shows a 'Resistor Color Code Chart' and an 'Activity: Reading a Resistor' worksheet. The chart is a table with columns for 'Color', '1st Digit', '2nd Digit', 'Multiplier', 'Tolerance', and 'Temperature Coefficient'. It lists colors from Black to White and their corresponding numerical values. The activity worksheet includes instructions for identifying resistors and a section for recording results.

Color	1st Digit	2nd Digit	Multiplier	Tolerance	Temperature Coefficient
Black	0				
Brown	1				
Red	2				
Orange	3				
Yellow	4				
Green	5				
Blue	6				
Violet	7				
Purple	8				
White	9				

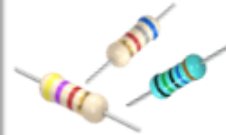




Activity

Reading a Resistor

What are resistor codes?

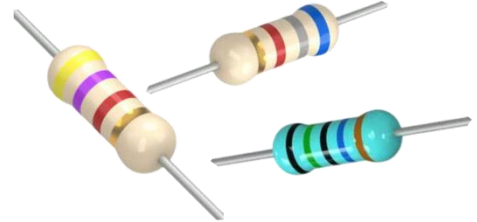- A standardized method to represent resistor values using color bands.



How do I identify which end of the resistor to start reading from?

- Many resistors have color bands grouped close together, or grouped closer toward one end. Hold the resistor with these grouped bands to your left.
- Always read resistors from left to right.
- Resistors never start with a metallic band on the left. If you have a gold or silver band on one end, you have a 5% or 10% tolerance resistor. Position this band on the right side, and start reading your resistor from the left to the right.
- On a four-band resistor, your third color will always be blue (106) or less.
- On a five-band resistor, your fourth color band will always be green (105) or less.

How do I decode color bands?

1. Identify the bands: (4 band, 5 band, or 6 band configurations)

For 4-band resistors

- 1st band: First digit of the resistance value
- 2nd band: Second digit of the resistance value
- 3rd band: Multiplier (power of ten)
- 4th band: Tolerance (accuracy)

For 5-band resistors

- 1st band: First digit of the resistance value
- 2nd band: Second digit of the resistance value
- 3rd band: Third digit of the resistance value
- 4th band: Multiplier (power of ten)
- 5th band: Tolerance (power of ten)

For 6-band resistors

- Same as 5-band plus
- 6th band: Temperature coefficient (ppm/K)

2. Map colors to values: Use the standardized color chart to find digits, multipliers, and tolerance. For example: Example: Red, Violet, Yellow, Gold → $27 \times 10,000 = 270,000 \Omega$ (270 k Ω \pm 5%).
3. Use the color code table: Black (0), Brown (1), Red (2), Orange (3), Yellow (4), Green (5), Blue (6), Violet (7), Gray (8), White (9), Gold = \pm 5%, Silver = \pm 10%, None = \pm 20%.


Part 1 – Small Group Practice

In small groups, use the ¹resistors provided by the instructor and the ²Resistor Color Code Chart handout to identify each resistor by reading its color bands. Use the space below to record the **digits, multiplier, tolerance**, and final **resistance** value.

Part 1 Work Space

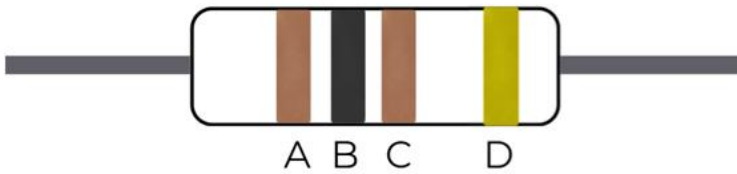
Part 2 – Independent Practice

On your own, read each resistor and use the space provided to note the digits, multipliers, and tolerance.



Colors: Brown, black, brown

1. _____

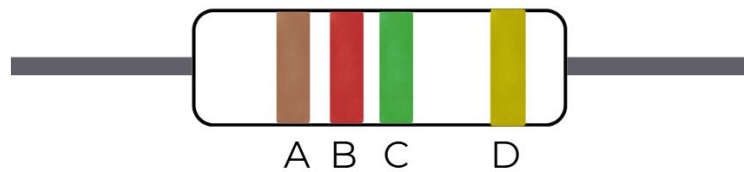

Colors: Brown, red, green, gold


2. _____

Module 4 – Circuit Components & Architecture




Colors: Yellow, purple, blue, black, brown

3. _____

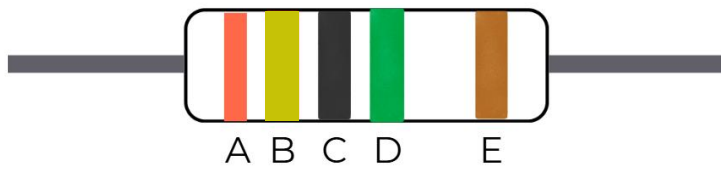

Colors: Orange, yellow, black, green, brown.

4. _____

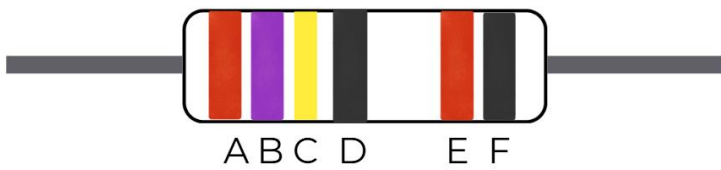


Colors: Red, purple, yellow, black, red, black.

5. _____


Diodes

- An electrical circuit device (semiconductor) that allows current to flow in one direction only
- Acts as a one-way gate for electricity
- Forward-Bias:
 - Anode is *more* positive than the cathode, current *flows* normally
- Reverse-Bias:
 - Anode is *less* than the cathode, diode *blocks* current

Diode



Diode Symbol



Anode (+) Cathode (-)


54

Notes:

- A **diode** is a semiconductor device that allows current to flow in one direction only.
 - It acts as a one-way gate for electricity, allowing current to move through the circuit in a single direction while blocking it from flowing in the wrong direction.
 - When the diode is **forward biased**, meaning the anode is *more* positive than the cathode, current **flows** normally.
 - When the diode is **reverse biased**, meaning anode is *less* positive than the cathode, the diode **blocks** current to protect the circuit and control how electricity moves.
-
-
-
-
-

Transistors

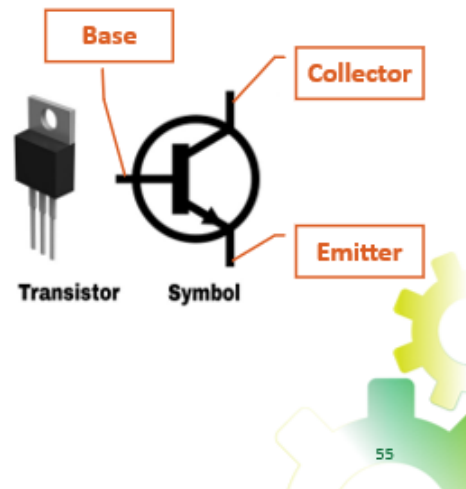- A semiconductor device used to amplify or switch electronic signals
- Acts like a relay but with no mechanical parts
- Composed of three terminals - Small input current or voltage at **base** controls larger current between **emitter** and **collector**




Notes:

- A **transistor** is a semiconductor device used to amplify or switch electronic signals.
 - When you apply voltage to the base it is like operating the relay coil, then power can flow from the collector to the emitter.
 - Advantage is no mechanical parts so there is little to no wear.
 - They act as an electronic switch/signal amplifier in circuits.
 - Transistors are composed of three parts: **Emitter**, **Base**, and **Collector**.
 - There will be a small input current or voltage at base controls larger current between emitter and collector.
-
-
-
-
-

Rectifiers

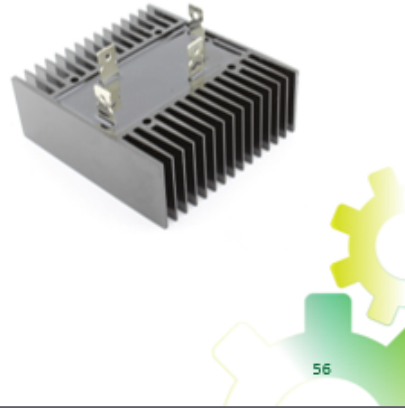- A device which converts electrical current starting in AC into DC
- Uses electric devices (usually diodes) to allow current to flow during a certain wave (e.g. positive and negative half-cycles)
- Applications include electronics, mobile phones, radio demodulation






Notes:

- A **rectifier** is a device which converts electrical current starting in AC into DC.
- They use electric devices (usually diodes) to allow current to flow during a certain wave (e.g. positive and negative half-cycles).
- Applications include electronics, cell phones, and radio demodulation.

Types of Rectifiers

Three Primary Types: Half-wave, Full-wave, Full-wave bridges

Feature	Half-Wave	Full-Wave	Bridge Rectifier
Diodes	1	2	4
Efficiency	Low	High	High

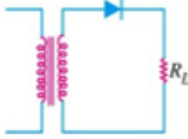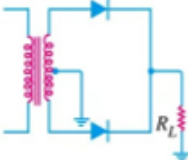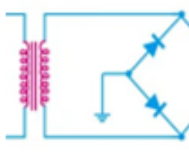
Notes:

- Now let's look at the three primary types of rectifiers, which are devices used to convert alternating current (AC) into direct current (DC). The three main types are half-wave rectifiers, full-wave rectifiers, and bridge rectifiers.
- The **half-wave rectifier**.
 - A half-wave rectifier uses one diode. It allows only one half of the AC waveform to pass through while blocking the other half.
 - Because only half of the waveform is used, the output DC is less efficient and more uneven.
- The **full-wave rectifier**.
 - A full-wave rectifier uses two diodes and a center-tapped transformer.
 - Instead of using only half of the AC signal, it converts both halves of the waveform into DC, which results in higher efficiency and a smoother output than the half-wave design.
- The **bridge rectifier**.
 - A bridge rectifier uses four diodes arranged in a bridge configuration.
 - This design also converts both halves of the AC waveform, but it does so without needing a center-tapped transformer.
 - Because of this configuration, bridge rectifiers are very common in power supplies and electronic devices.

Module 4 – Circuit Components & Architecture

Inductors

- Electrical device that stores energy in a **magnetic field**
- Made by winding insulated wire into a coil
- Also called a coil, reactor, or choke
- Opposes sudden changes in current
- Used to smooth signals and reduce current spikes




The image displays six different types of inductors arranged in a 3x2 grid. Each inductor is labeled with its name: Multilayer Ceramic Inductor (a rectangular component with a central slot), Ferrite-Core Inductor (a toroidal core with a wire wound around it), Air-Core Inductor (a simple wire coil), Iron-Core Inductor (a wire coil wound around a cylindrical iron core), Bobbin Based Inductor (a wire coil wound around a cylindrical bobbin), and Variable Inductor (a wire coil wound around a cylindrical core with a sliding contact for adjusting inductance). A green arrow points to the bottom right corner of the image, and the number 58 is visible in the bottom right corner.

Notes:

- An **inductor** is an electrical device that stores energy in a magnetic field.
 - Unlike a capacitor (which stores energy in an electric field) an inductor stores energy *magnetically*.
 - Inductors are typically made by winding insulated wire into a coil.
 - When current flows through that coil, it creates a magnetic field around it.
 - That magnetic field is where the energy is temporarily stored.
 - You may also hear inductors referred to as a **coil**, a **reactor**, or a **choke**, depending on the application.
 - One of the most important functions of an inductor is that it resists sudden changes in current.
 - When current tries to increase or decrease quickly, the inductor reacts by opposing that change.
 - This makes inductors useful for:
 - Smoothing electrical signals
 - Reducing electrical noise
 - Limiting sudden current spikes
 - In power systems and electronics, inductors help stabilize circuits and protect components from abrupt current changes.
 - Inductors have little to no effect on DC and do have many functions in AC circuits.
-
-
-
-
-

Capacitors

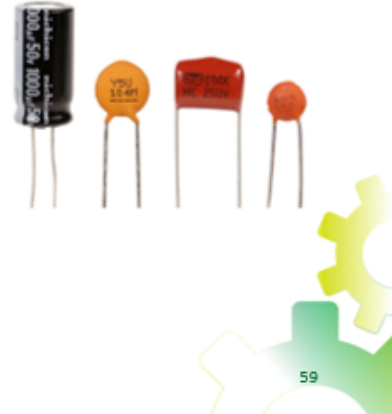- Electrical device that stores energy in an **electric field** and releases energy as needed
- Made of two conductors separated by an insulating material (dielectric)
 - In **DC** circuits: charges, then blocks further current flow
 - In **AC** circuits: continuously charges and discharges




Notes:

- A **capacitor** is an electrical device that stores energy in an electric field.
- It consists of two conductive plates separated by an insulating material called a dielectric.
- When voltage is applied, the capacitor stores energy by building up an electric charge between the two plates. That stored energy can then be released back into the circuit when needed.
- In a **DC circuit**, a capacitor will charge up to the applied voltage and then block further current flow once it is fully charged.
- In an **AC circuit**, the voltage is constantly changing direction. Because of that, the capacitor continuously charges and discharges, allowing energy to keep moving through the circuit.
- Capacitors are commonly used for:
 - Smoothing voltage
 - Filtering noise
 - Stabilizing power supplies
 - Timing and signal processing applications

Transformers

An electrical circuit device that uses electromagnetic induction to transfer energy from one circuit to another

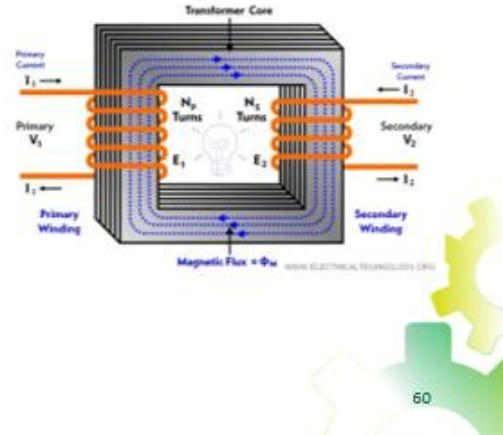- Types include **step-up** and **step-down**
- Applications:
 - Audio and radio systems
 - Power Supplies
 - Power Transmissions




Notes:

- **Transformers** are an electrical circuit device that uses electromagnetic induction to transfer energy from one circuit to another.
- The primary types include step-up and step-down transformers.
- A **step-up transformer** is designed to increase the voltage from primary to secondary.
- A **step-down transformer** is designed to decrease the voltage from primary to secondary.
- Applications for a transformer can include:
 - Audio and radio systems
 - Power Supplies
 - Power Transmissions

Sensors

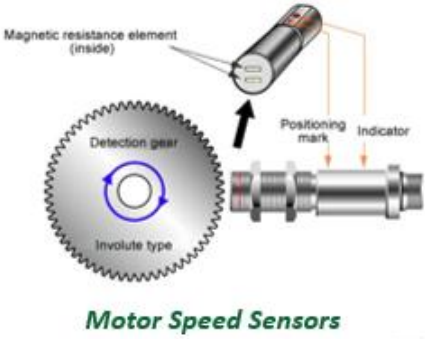- Device that detects changes in electrical or physical conditions
- Converts those changes into a usable electrical signal
- Primary Types:
 - Mechanical & Pressure
 - Thermal
 - Magnetic & Electromagnetic
 - Chemical



Motor Speed Sensors

61

Notes:

- A **sensor** is a device that detects changes in conditions — such as motion, temperature, pressure, light, or electrical fields — and converts that change into a usable **electrical signal**.
 - In simple terms, a sensor takes a physical event and turns it into information a circuit or control system can understand.
 - For example:
 - A temperature sensor detects heat and converts it into a voltage signal.
 - A pressure sensor detects force and converts it into an electrical output.
 - A magnetic sensor detects movement or position and generates a signal.
 - Sensors are critical in modern electrical and transportation systems because they allow systems to monitor, adjust, and respond automatically.
-
-
-
-
-

Knowledge Check



Why does circuit protection matter?

62

Knowledge Check



Match the key term with the correct description.

- | | |
|---------------|--|
| 1. Relay | A. Allows current to flow in only one direction. |
| 2. Switch | B. Completes or breaks a circuit by allowing or preventing current flow. |
| 3. Diode | C. An electromechanical device that uses a low-power signal to control a higher-power circuit. |
| 4. Transistor | D. A semiconductor device used to amplify or switch electronic signals. |

63

Knowledge Check



Walk us through reading a resistor using the image below.
Calculate the final resistance.



64

Knowledge Check



What is a capacitor?

A.) A device that converts AC current into DC current

B.) A device that transfers energy between circuits using electromagnetic induction

C.) An electrical device that stores energy in an electric field

D.) A device that allows current to flow in only one direction

65

Knowledge Check



What is a rectifier?

A.) A device that stores energy in an electric field

B.) A device that converts electrical current from AC to DC

C.) A device that transfers energy between circuits using electromagnetic induction

D.) A device that allows current to flow in only one direction

66

Knowledge Check



What is the difference between a step-up and step-down transformer?

67

Knowledge Check



A _____ is a device that detects changes in conditions such as motion, temperature, pressure, light, or electrical fields and converts that change into a usable electrical signal.

A.) Relay

B.) Electromagnet

C.) Transformer

D.) Sensor

68

Summary and What's Next


- ✓ Power sources supply energy to the circuit.
- ✓ Wires carry electricity between components.
- ✓ Loads use electrical energy to do work.
- ✓ Protection devices keep circuits and equipment safe.
- ✓ Control devices turn power on and off automatically.
- ✓ Electronic components change and control how electricity flows.

Next, we'll see how circuit components are represented on electrical diagrams.

69

Notes:

- We started by looking at **power sources**, which supply the energy that moves through a circuit.
 - We discussed how **wires** act as the pathway, carrying electrical current between components.
 - Then we looked at **loads**, which use electrical energy to perform work — whether that's producing light, motion, or heat.
 - We also covered **protection devices**, which safeguard circuits and equipment from faults like overcurrent or short circuits.
 - Next, we explored **control devices**, which allow circuits to turn on and off automatically.
 - And finally, we introduced **electronic components** that regulate and shape how electricity flows through a system.
 - **The key takeaway is this:** Every electrical system is made up of components that generate, carry, control, protect, and use electrical energy. Now that we understand the function of these parts, the next step is learning how they are represented visually.
 - **Next, we'll see how circuit components are represented on electrical diagrams.**
-
-
-
-
-

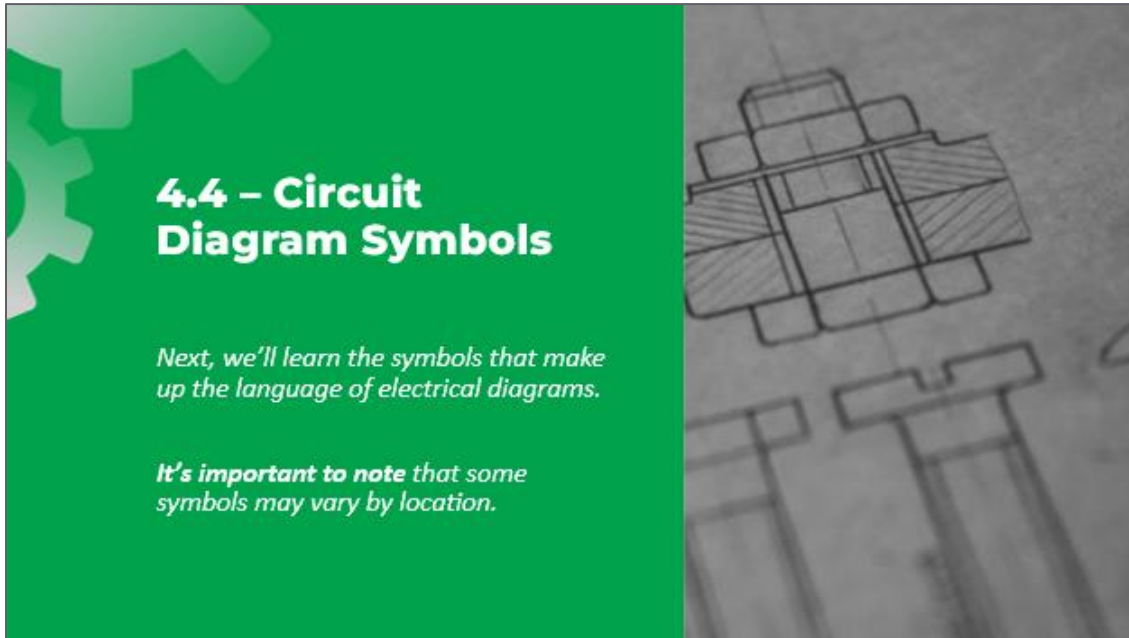

Notes:

- Now that you know the parts of a circuit, let's see how those parts are shown on electrical diagrams.

Why Electrical Symbols Matter

Electrical Diagrams use **symbols** instead of pictures.

Symbols are a shared language that technicians use to show:

- Type of component
- Connection
- How electricity moves through the system

Learning symbols allows you to read any electrical diagram, even if you've never seen that system before.

71


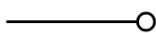
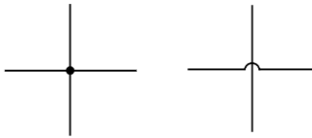
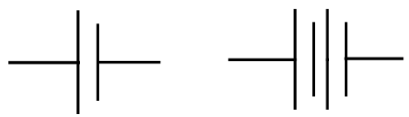
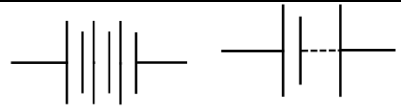







Notes:

- Electrical Diagrams use **symbols** instead of pictures.
- Think of symbols like road signs. You don't need a picture of a stop sign to know what it means, the shape and color tell you what to do.
- Electrical symbols work the same way. Once you know them, you can look at any diagram and understand what parts are in the circuit and how they're connected.
- Symbols are a shared language that technicians use to show the type of component, their connection within the system, and how electricity moves through the system.
- Learning symbols allows you to read any electrical diagram, even if you've never seen that system before.

 **Resource**


Diagram Symbols

The chart below shows different types of symbols you may see on a diagram. Use “Other” category to record any agency specific symbols.

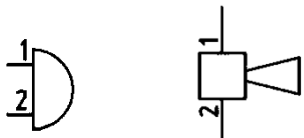Category	Type	Symbol
Connection Points	Conductor/Wire	
	Terminal	
	Connected Wire; Not Connected Wire	
Power Source (Battery)	Single Cell, Double cell	
	Three Cell, Multiple Cell	
Switch	Open Switch, Closed Switch	
Circuit Protection	Circuit Breaker	
	Fuse	
Load	Motor	DC  AC 
	Bulb	
	Bell/Buzzer, Horn	


Module 4 – Circuit Components & Architecture

	LED Lamb, Incandescent Lamp	
Diode	Standard diode	
Relay	Common Relay Symbol	
Resistor	Resistor, Variable Resistor	
Capacitor	Standard Capacitor	
Inductor	Air Core, Iron Core	
	Ferrite Core, Variable Core	
Transformer	Standard transformer	
	<i>Other:</i>	
OTHER		

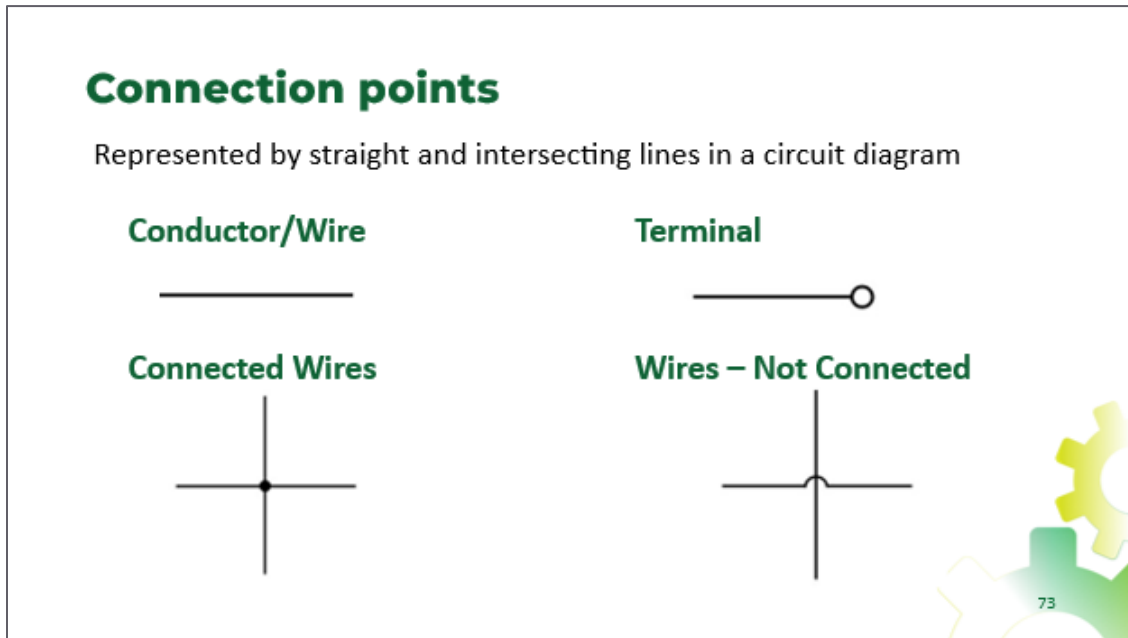


Notes:

- In schematics, connections are shown using straight lines to represent conductors or wires.
- A simple straight line represents a **conductor** — the pathway for current to travel.
- A **terminal** is shown as a line ending in a small circle. That circle indicates a connection point where a wire connects to a device or component.
- When wires are **connected**, you will see a solid dot at the intersection. That dot indicates an electrical connection — current can flow between those conductors.
- When wires are **not connected**, one wire will typically “jump” over the other using a small arc. That shows the wires cross visually, but they are not electrically connected.
- This distinction is critical when reading diagrams. Missing or misreading a connection dot can completely change how a circuit functions.

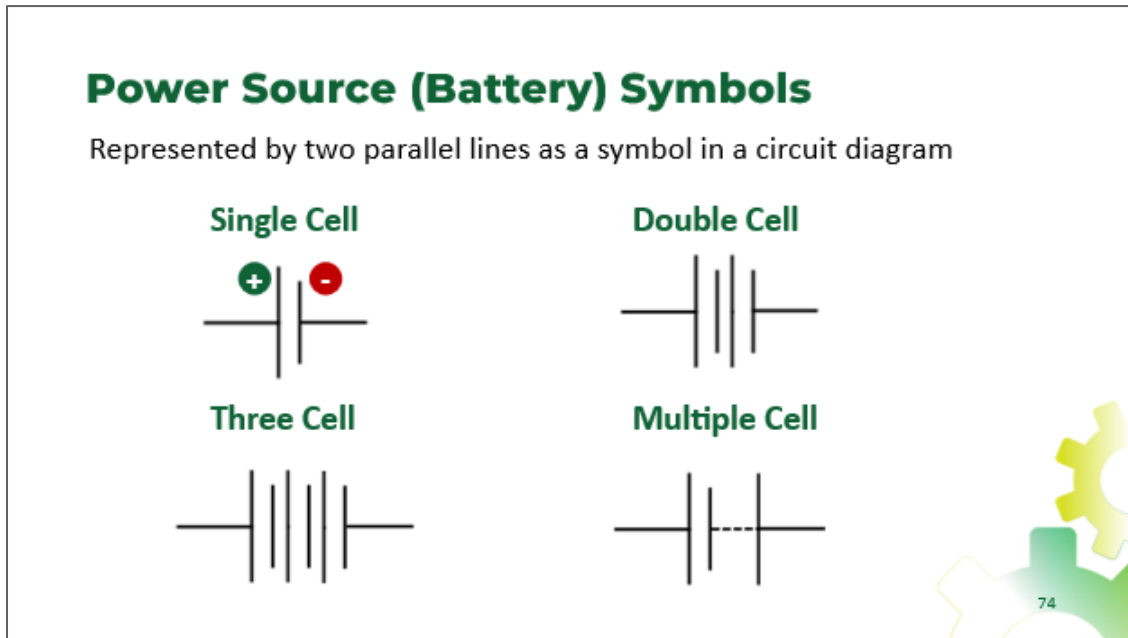

Notes:

- A battery or DC power source is shown using **two parallel lines**.
 - One line is longer, and one line is shorter.
- The **longer line represents the positive terminal**, and the **shorter line represents the negative terminal**.
 - That length difference is important — it tells you polarity.
- There are a few types of batteries represented on this slide:
- **Single Cell** - A single cell has one long line and one short line. This represents one voltage source — like a single battery cell.
- **Double Cell** - A double cell symbol shows two sets of long and short lines. Each pair represents another cell added in series. More cells mean higher total voltage.
- **Three Cell** - With three sets of long and short lines, you have three cells in series. Each additional cell increases the total voltage supplied to the circuit.
- **Multiple Cell** - The multiple-cell symbol is often simplified with dashed or abbreviated lines. Instead of drawing every cell individually, the diagram shows that there are multiple cells connected in series. This keeps complex diagrams cleaner while still communicating that multiple voltage sources are present.

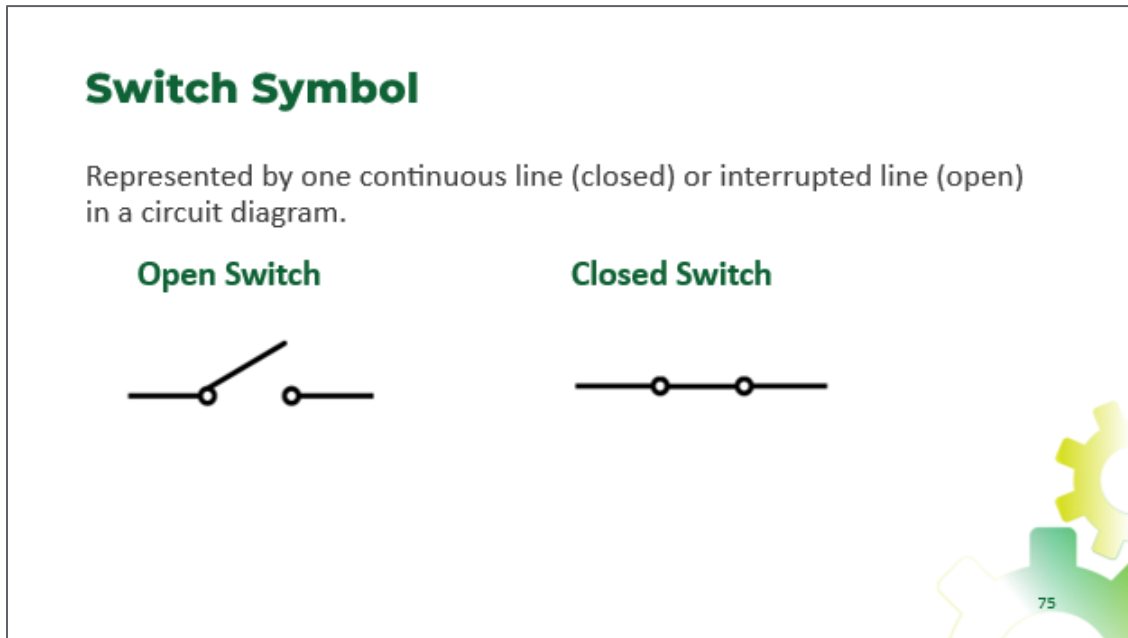


Notes:

- A switch is shown as either a continuous line or an interrupted line, depending on its position.
- An **open switch** is shown with a gap in the line. That gap indicates the circuit is broken, and current cannot flow.
- When a switch is open, the path is interrupted — just like turning a light switch off.
- A **closed switch** is shown as a continuous line. This means the circuit path is complete, and current is allowed to flow.
- When a switch is closed, electricity can move through the circuit and power the load.
- There are other examples that may be specific depending on the setup of a circuit. On the right you will see two agency specific switch symbols used at CATS (Charlotte Area Transit System).

Circuit Protection Symbols


- **Circuit Breaker** – Represented by a curved line ended with two circles
- – Represented by box with line running through OR curved “S” line ended with two circles

Circuit Breaker

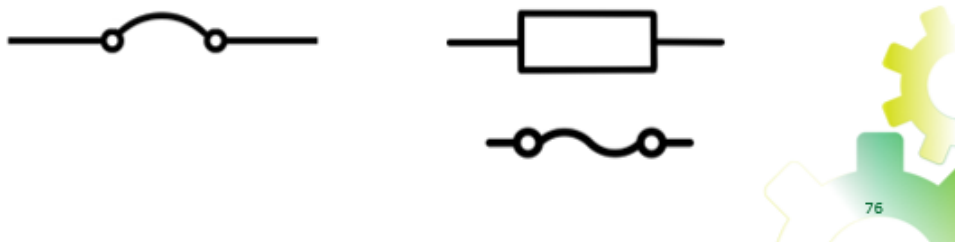

Notes:

- Now let’s look at how circuit protection devices are represented on electrical diagrams.
- First, the **circuit breaker** symbol is:
 - A circuit breaker is typically shown as a curved line between two connection points, often ending in small circles.
- This symbol represents a protective device that can open the circuit automatically if current exceeds a safe limit.
- Unlike a , a circuit breaker can usually be reset after the fault is cleared.
- Next, the symbol. May be represented in one of two common ways:
 - A rectangular box with a line running through it or a curved “S” shaped line between two connection points
 - Both symbols represent a device designed to protect the circuit from overcurrent.
- When excessive current flows, the element melts, permanently opening the circuit.
- Unlike a breaker, a must be replaced after it operates.

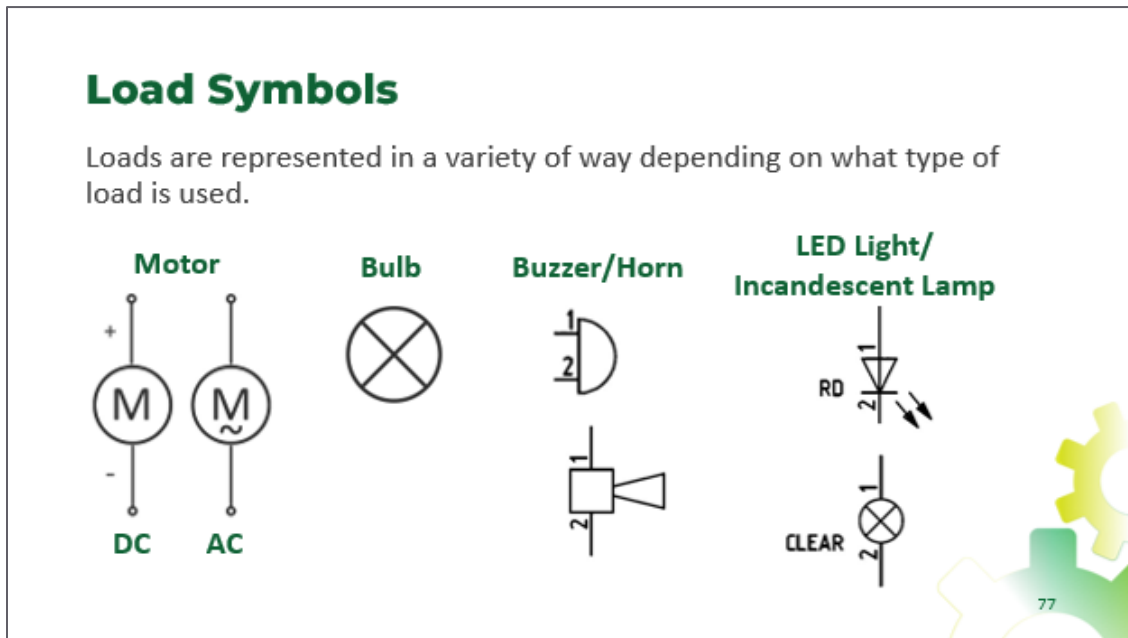

Notes:

- Next, Now let's look at how loads are represented on electrical diagrams.
- Loads can appear in different forms depending on what the circuit is powering. The symbols may vary slightly depending on the agency or application, but the core representations remain consistent.
- **Motors (DC and AC)**
 - The symbols shown here represent both DC motors and AC motors.
 - DC voltage is commonly supplied by batteries or DC power supplies.
 - AC voltage typically comes from wall outlets in homes and facilities.
 - On schematics, DC motors are usually marked clearly, and AC motors may include a small sine wave symbol to indicate alternating current.
- **Light Bulb**
 - In this module, we'll often focus on a basic load like a light bulb.
 - The standard symbol for a bulb is a circle with an "X" inside.
 - This represents a simple resistive load that converts electrical energy into light and heat.
- **Buzzer or Horn**
 - The buzzer or horn symbol represents an audible load — something that produces sound. These are common in alarms, signaling systems, and warning circuits.
- **LED / Incandescent Lamp**
 - LEDs have a distinct symbol showing a diode with arrows pointing outward, representing light emission.
 - An incandescent lamp uses the circular "X" symbol, similar to a general bulb.
 - The labels may indicate color, such as RD for red or CLEAR for standard incandescent.

Module 4 – Circuit Components & Architecture


Diode Symbols

Represented by a triangle pointing toward a vertical line. The vertical line represents the cathode.



Notes:

- The symbol for a **diode** is a triangle pointing toward a vertical line. The triangle represents the anode, and the vertical line represents the cathode.
- On a schematic, the diode symbol shows the direction conventional current is allowed to flow — from anode to cathode.
- Diodes control and protect circuits by allowing current to flow in one direction while blocking reverse current.
- When you see a diode symbol, pay close attention to its orientation, especially during troubleshooting, because current can only flow in one direction.

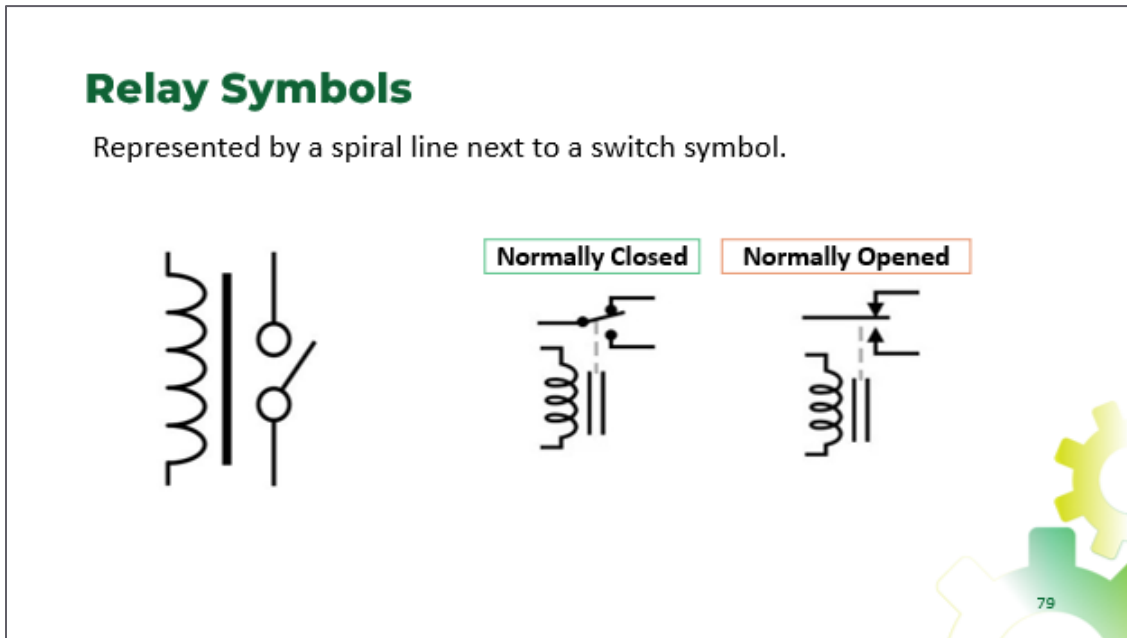






Notes:

- What symbol do you see here that we have already talked about?
- A relay symbol typically consists of two main parts:
 - A **coil**, shown as a spiral or curved line.
 - One or more **switch contacts**, shown using standard switch symbols.
- The coil represents the electromagnet inside the relay.
- When current flows through the coil, it creates a magnetic field. That magnetic field mechanically moves the switch contacts.

Resistor Symbols


Represented by a zigzag line or rectangle. If it has an arrow, it is a variable resistor.

US Schematics	International Schematics
	
	




Notes:

- Resistors are typically shown in one of two standard formats.
 - The first is a **zigzag line**. This is the common symbol used in many U.S. schematics.
 - The second is a **rectangle**. This version is often used in international or IEC-style diagrams.
- Both symbols represent the same component — a fixed resistor.
- A **variable resistor** will have an **arrow crossing the resistor symbol**, which indicates it is adjustable.
- The arrow represents the movable contact that changes the resistance value.
- Variable resistors are used when you need to adjust current or voltage levels in a circuit — for example, in volume controls or tuning circuits.

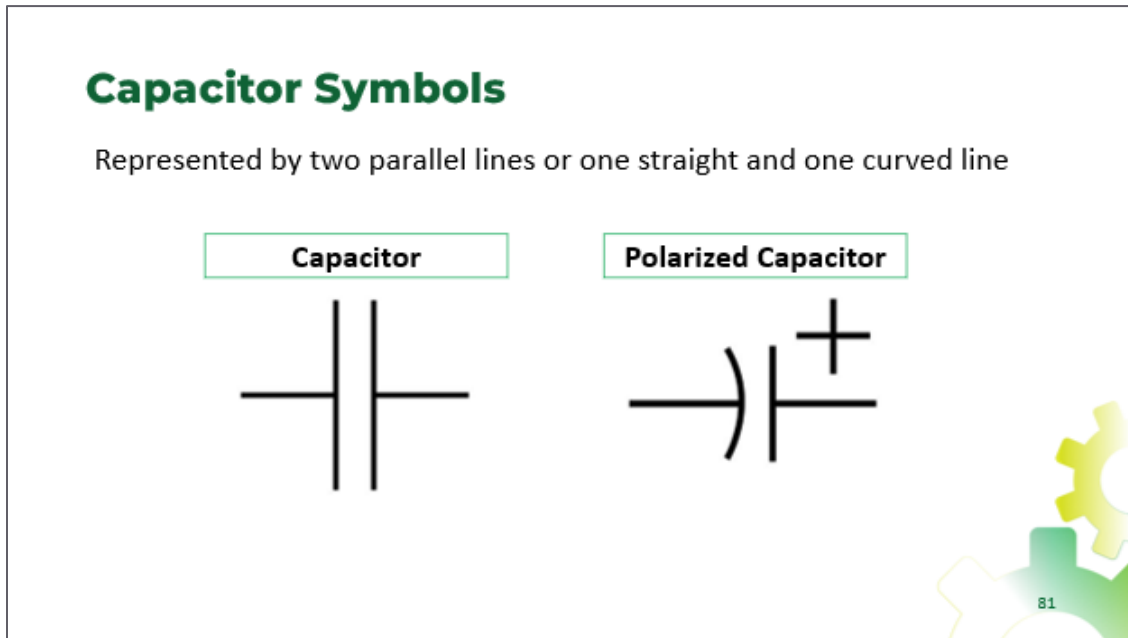

Notes:


- The symbol for a capacitor is shown as **two parallel lines**. Those lines represent the two conductive plates inside the device.
- Sometimes, you'll see one straight line and one curved line.
 - This typically represents a **polarized capacitor**, where orientation matters. The curved plate often indicates the negative side, and you may see a plus sign marking the positive terminal.
 - As mentioned earlier in the module, the function of a capacitor is to **store and release electrical energy**.
- Capacitors store energy in an electric field created between those two plates.
- When reading a schematic, the **capacitance value** listed next to the symbol tells you how much energy the capacitor can store and release at a given voltage.
- Understanding this relationship helps you predict how the capacitor will behave in a circuit.

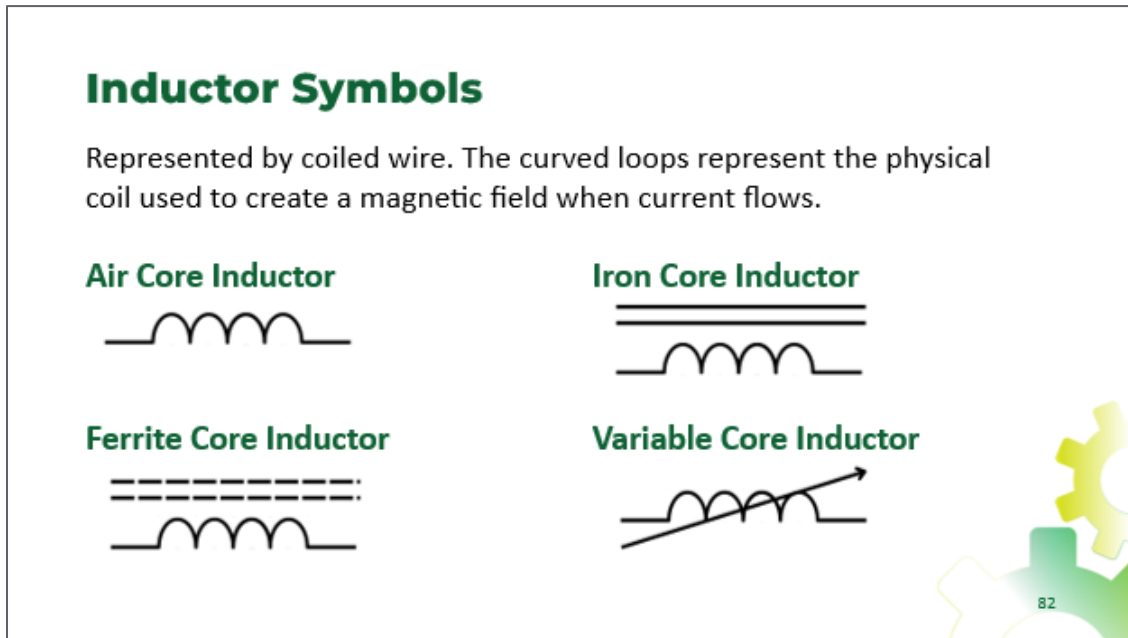

Notes:

- The symbol for an inductor is a **coiled wire**. The curved loops represent the physical coil used to create a magnetic field when current flows.
- As mentioned earlier in the module, the primary function of an inductor is to **store energy in a magnetic field**.
- When current flows through the coil, a magnetic field forms around it. That magnetic field is where the energy is temporarily stored.
- This slide shows a few different types of inductors.
- **Air Core Inductor**
 - The basic inductor symbol — just the **coil** — usually represents an air core inductor.
 - This means there is no magnetic core material inside the coil. The magnetic field is created in open air.
 - Air core inductors are common in high-frequency applications.
- **Iron Core Inductor**
 - When you see **solid parallel lines** next to the coil, that indicates an iron core inductor.
 - The solid lines represent a ferromagnetic core placed inside the coil.
 - Adding an iron core increases the inductance by strengthening the magnetic field.
- **Ferrite Core Inductor**
 - If the parallel lines appear **dashed**, that typically represents a ferrite core.
 - Ferrite materials are commonly used in electronics because they perform well at higher frequencies and reduce energy losses.
- **Variable Core Inductor**
 - If an adjustable core, which allows the inductance value to be changed.
 - These are often used in tuning circuits, such as radios or signal processing systems.

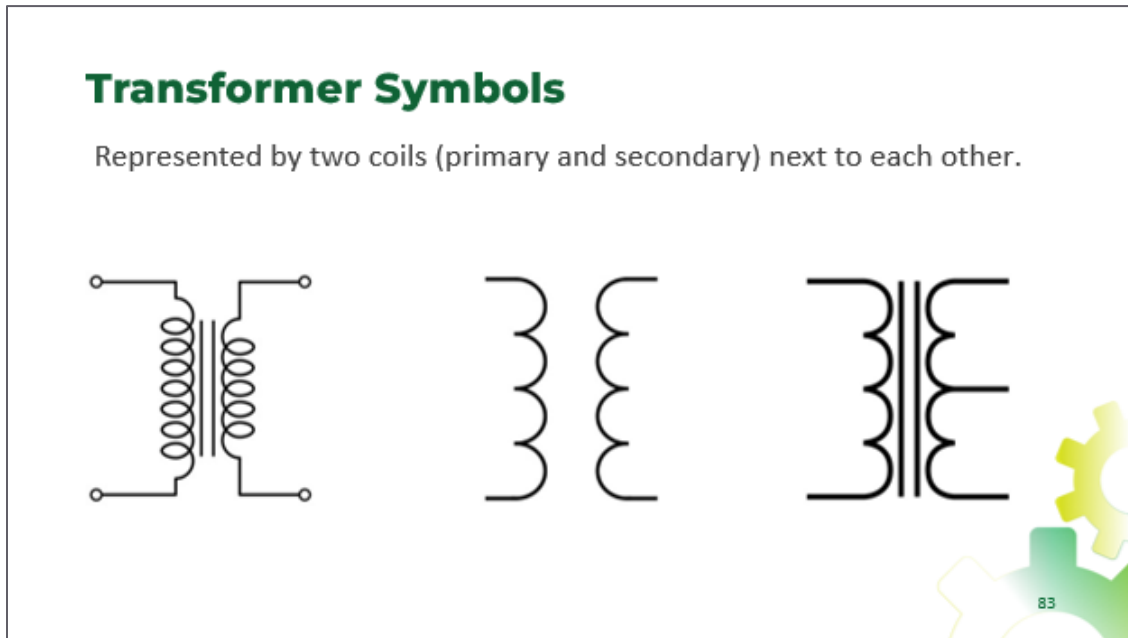Module 4 – Circuit Components & Architecture



Notes:

- A **transformer** symbol consists of two coils placed next to each other.
- One coil represents the primary winding, and the other represents the secondary winding.
- The key idea is that these two coils are magnetically coupled but not electrically connected.
- Energy is transferred from the primary to the secondary through electromagnetic induction.
- Sometimes you'll see the two coils drawn without any lines between them.
- Other times, you'll see parallel vertical lines between the coils.
- Those lines represent a magnetic core — usually iron — that helps strengthen and guide the magnetic field between the windings.
- So then:
 - Two coils side-by-side = transformer
 - Lines between them = magnetic core

Activity – Circuit Symbols Practice



Working in teams, select 4-6 circuit components from the resource chart. Create a simple circuit using the correct symbols. Label each symbol.

Identify:

- ✓ Power source
- ✓ Load(s)
- ✓ Control device
- ✓ Protection device
- ✓ Whether the circuit is series, parallel or series-parallel

Be prepared to explain your circuit to the class.



84

Notes:

- After the activity, answer the following debrief questions:
 - Which symbols appeared most frequently in your circuits?
 - How did you determine whether your circuit was series, parallel, or series-parallel?
 - Why is it important for technicians to use standardized symbols instead of drawings or pictures?
 - How do symbols make electrical diagrams easier to read and troubleshoot?

Key Takeaway:


Electrical symbols provide a standardized language that allows technicians to quickly understand, communicate, and troubleshoot electrical circuits regardless of the equipment or manufacturer.

Knowledge Check



What does this image represent?

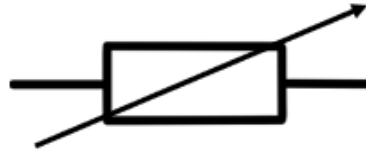- A. Variable resistor
- B. Transformer
- C. Inductor
- D. Diode




85

Knowledge Check



What does this image represent?

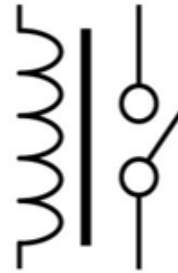- A. Closed circuit
- B. Relay
- C. Load symbol
- D. Circuit protection



86

Summary

- Symbols are a shared language used in electrical diagrams
- Each symbol represents a specific circuit component.
- Symbols show how parts are connected and how power flows.
- Knowing symbols lets you read any electrical diagram.




87

Notes:

- Symbols are a shared language used in electrical diagrams. No matter the system, these symbols allow technicians, engineers, and electricians to communicate clearly.
- Each symbol represents a specific circuit component. When you see a symbol, you should immediately recognize the type of device and its function.
- Symbols don't just show components — they show how parts are connected and how power flows through the system.
- Once you understand the symbols, you can read and interpret electrical diagrams with confidence.
- That ability is critical for troubleshooting, installation, and system analysis.
- As we move forward, we'll begin applying these symbols in full diagrams so you can practice identifying components and understanding how entire systems operate.

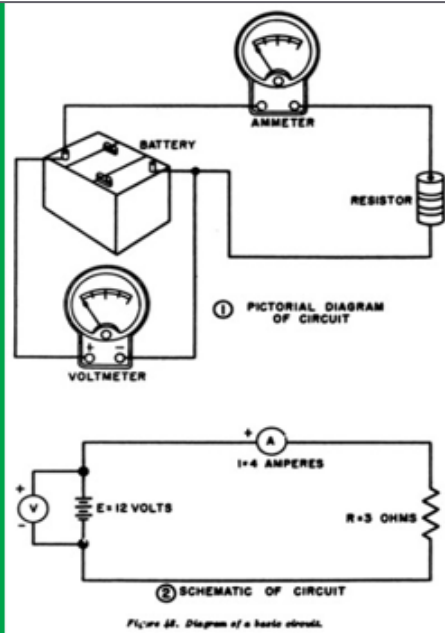4.5 – Electrical Circuit Diagrams

Now that we've learned the common electrical symbols used in schematics, let's see how those symbols are combined to create electrical circuit diagrams.



Notes:

- Now that we've learned the common electrical symbols used in schematics, let's see how those symbols are combined to create electrical circuit diagrams.

Why Electrical Diagrams Matter

Before working on any electrical system, technicians need a way to see how it is put together.

Electrical Diagrams are like maps that show:

- ✓ Where power comes from
- ✓ Where it goes
- ✓ What components are in between

Diagrams help you understand a system before you touch it, making work safer and more accurately.

89

Notes:

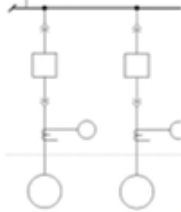
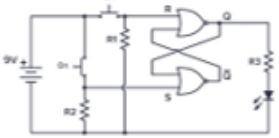

- You will not yet be using diagrams to fix things, that comes later after more advanced training. Right now, diagrams help to guide your understanding.
- You will learn about where power comes from, where it goes, and what components are used in the different systems we will discuss.
- A common question you might ask is: What is this system made of and how is it connected?
- Understanding a system before you even touch it, will help improve your safety, communication, and understanding what you're looking at when you open a cabinet or panel.
- Electrical diagrams are similar to maps. They are a visual representation of an electrical system, usually with a map or drawing that shows a circuit's layout of components, positions and connections.


Electrical Circuit Diagrams

Visual representations of an electrical system that shows a circuit's layout of components, positions and connections

Common types :

Block Diagrams	Schematics	One Line Diagrams
-----------------------	-------------------	--------------------------






Notes:

- Before a technician works on a system, they need a way to see how it's put together.
- Electrical diagrams show where power comes from, where it goes, and what's in between.
- An **electrical circuit diagrams** are visual representations of an electrical system, usually with a map or drawing that shows a circuit's layout of components, positions and connections.
- Primary types of electrical circuit diagrams can include the following:
 - Block diagrams
 - Schematics
 - One-line diagrams (also called single-line diagrams)

Block Diagrams

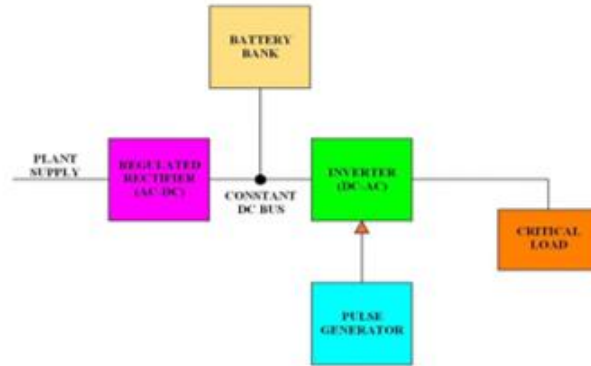A diagram of a system where main parts and functions represented by blocks connected by lines to show relationships between them.




91

Notes:

- A **block diagram** is a diagram of the system in which the principal parts or functions are represented by blocks connected by lines that show the relationships of the blocks.
- You should consider the block diagram a more general, less detailed description of the electrical system that is aimed more at understanding the overall concepts and less at understanding the details of circuit operation.
- What does it help you do?

One-Line Diagram

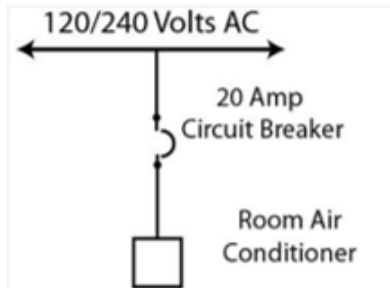A diagram of a system where single lines and symbols are used to represent system components and connections.



Notes:

- A **one-line diagram** also known as a single-line diagram is a simplified notation for representing an electrical system.
- The one-line diagram is similar to a block diagram except that electrical elements such as switches, circuit breakers, transformers, and capacitors are shown by standardized schematic symbols.
- A one-line diagram uses simple symbols and a single line to show how major electrical components are connected.
- These diagrams focus on the overall flow of power, rather than showing detailed wiring.
- You can familiarize yourself with the electrical system by using these simple, no-frills diagrams.
- What does it help you do?


Schematics

A diagram of a system that shows simplified standard symbols of the connections between devices.

The image contains two circuit diagrams. The left diagram is a simple AC circuit showing a power source (E) connected to a 20 Amp Circuit Breaker, which is connected to a load (R). The circuit is completed by a conductor (Pathway for Current). The right diagram is a more complex schematic showing a 9V battery connected to a network of resistors (100 Ohms, 10 Ohms), capacitors (C 100F), and a transistor.

Notes:

- A **schematic** is a diagram that shows the components of the circuit as simplified standard symbols showing the connections between the devices including power and signal connections.
- The arrangement of the components interconnections on the diagram does not correspond to their physical locations in the finished device.
- What are schematics used for? What does it help you do?
- When have you seen schematics used?
- What does it help you do?

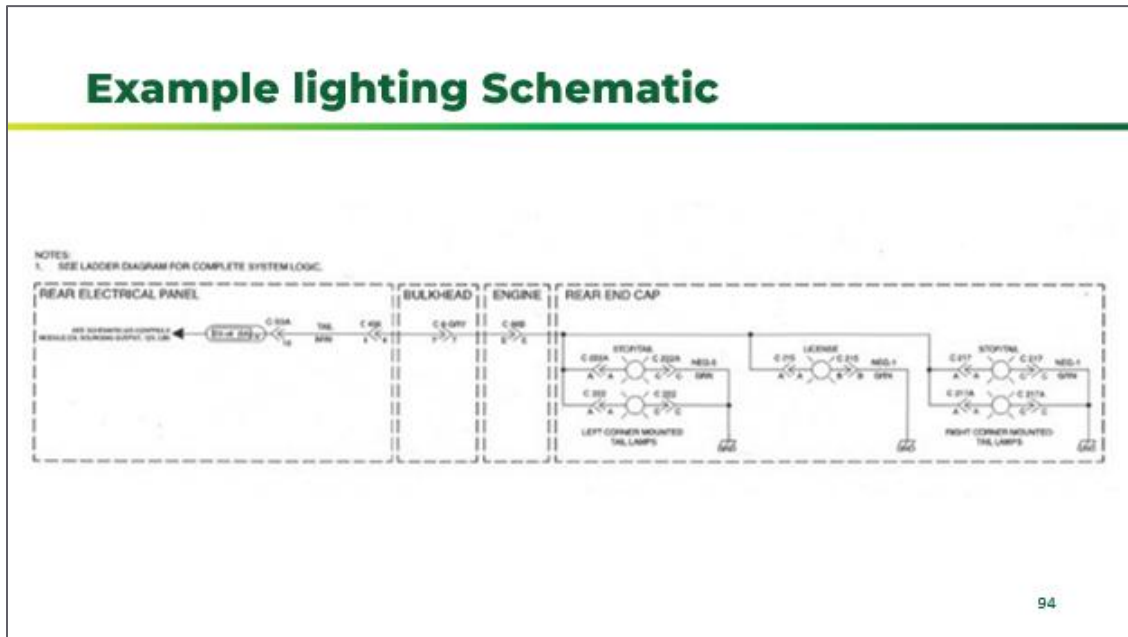

Notes:

- Up to this point, we've been working with simplified circuits to learn how current flows and how components are connected.
- Real-world schematics are more detailed, but they follow the same electrical principles.
- This diagram shows several lighting circuits located at the rear of a bus, including tail lights, stop lights, and license plate lighting.
- Notice that multiple lighting circuits are connected to the same power source while operating independently. This is an example of parallel circuit design.
- Individual lamps within a branch may be connected in a way that creates a series or series-parallel arrangement.
- Understanding series, parallel, and series-parallel circuits helps technicians predict how a system will behave when a component fails.
- For example, if one lighting branch fails, other branches may continue to operate because they have their own current path.
- Technicians use schematics like this to trace power, identify components, and troubleshoot faults efficiently.

- Can you identify any parallel branches in this diagram?
- Why do you think vehicle lighting systems are commonly designed using parallel circuits?
- How would this diagram help a technician troubleshoot an inoperative light?

Module 4 – Circuit Components & Architecture

Key Takeaway:

Although real-world schematics appear more complex than the examples we've practiced, they are built from the same series, parallel, and series-parallel circuit concepts. Understanding those foundational concepts makes larger diagrams much easier to read and troubleshoot.

Trace the Circuit

Directions:

1. Start at the battery (+)
2. Follow the path current takes through the circuit
3. Identify
 - ✓ Power source
 - ✓ Circuit protection device
 - ✓ Switch
 - ✓ Load
 - ✓ Ground

95


Notes:

- Current leaves the **battery positive terminal**, which serves as the power source for the circuit.
- Current travels through the **fuse**, which protects the circuit from excessive current.
- Current then reaches the **switch (S1)**.
- When the switch is closed, current continues to the **headlight (L1)**.
- The headlight acts as the **load**, converting electrical energy into light.
- Current returns through the **ground path** to complete the circuit.
- When troubleshooting, technicians trace the flow of current from the source to the load and back to the source to identify where the circuit has been interrupted.

- Which component is the power source?
- Which component provides circuit protection?
- Which component controls current flow?
- Which component is the load?

Key Takeaway:

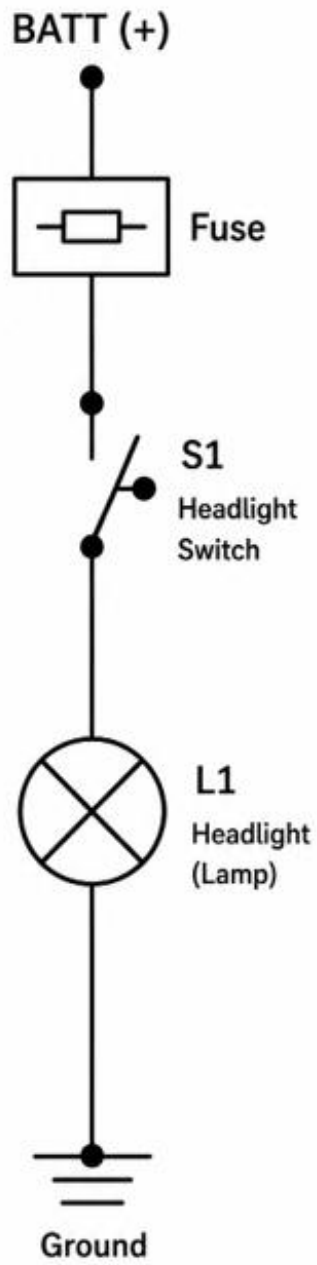
Electrical troubleshooting begins by tracing the path of current through the circuit and identifying where that path is interrupted.



Trace the Circuit – Guided Practice

Directions:

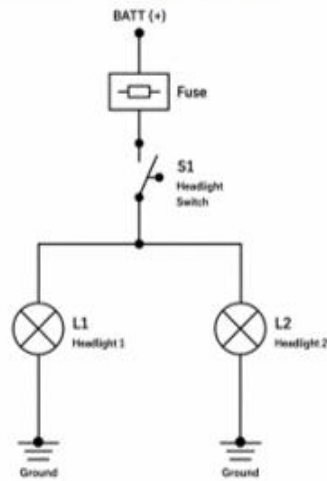1. Start at the battery (+)
2. Trace the path of current when the switch is closed
3. Identify
 - ✓ Power source
 - ✓ Circuit protection device
 - ✓ Control device
 - ✓ Switch
 - ✓ Loads
 - ✓ Return path




Notes:

- Current leaves the battery positive terminal and travels through the fuse.
 - The fuse protects the circuit from excessive current.
 - Current reaches switch S1.
 - When S1 closes, current can flow into the circuit.
 - At the junction, current has two paths available.
 - One path supplies Headlight 1 (L1).
 - The second path supplies Headlight 2 (L2).
 - This is a **parallel circuit** because both loads are connected across the same source voltage.
 - After passing through each headlight, current returns to the battery through its ground connection.
 - Because the headlights are connected in parallel, each lamp can operate independently of the other.
-
- Where does current originate?
 - What component protects the circuit?
 - What component controls current flow?
 - What type of circuit is shown?
 - Why are there two paths for current?
 - What happens when the switch closes?

Key Takeaway:

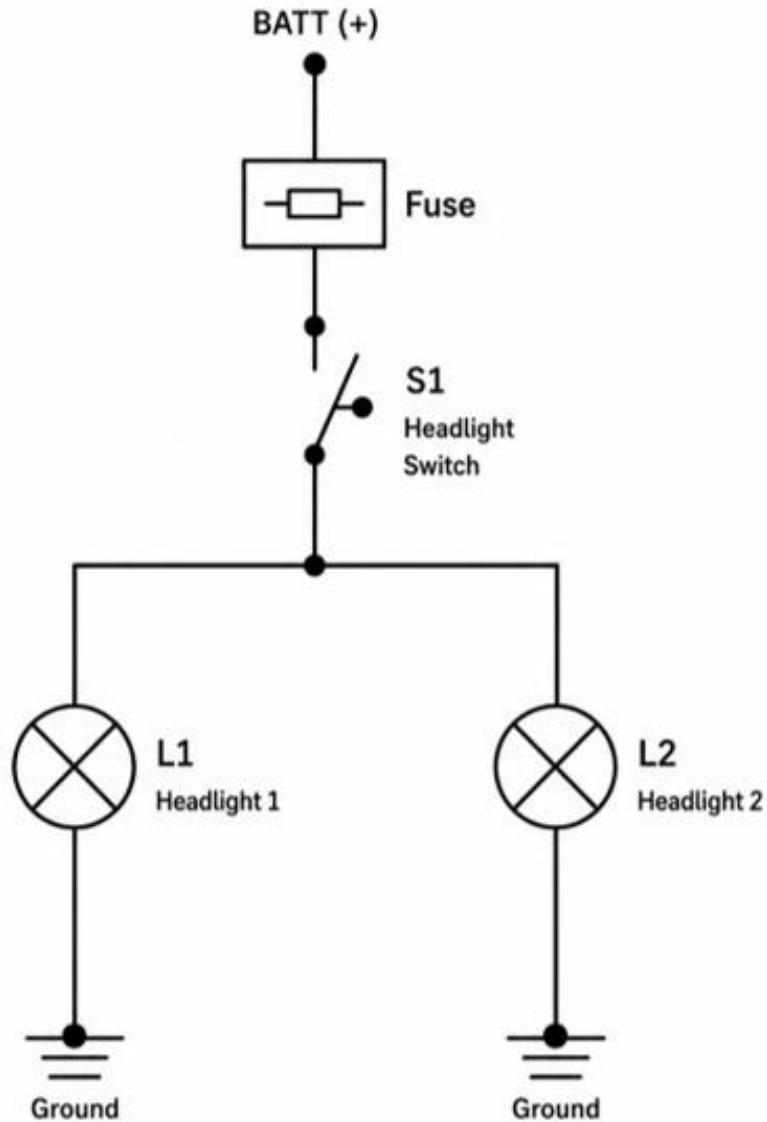
In a parallel circuit, current has multiple paths. A failure in one branch does not necessarily stop current flow through the remaining branches. This is one reason many vehicle lighting circuits are designed using parallel connections.



Activity: Trace the Circuit

Directions:

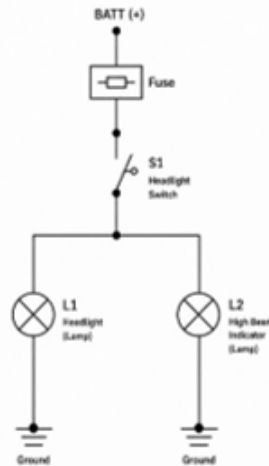1. Start at the battery (+)
2. Trace the path of current when switch S1 is closed
3. Identify
 - ✓ Power source
 - ✓ Circuit protection device
 - ✓ Control device
 - ✓ Load #1
 - ✓ Load #2
 - ✓ Return path
4. Optional troubleshooting scenarios



97

Notes:

Remember the following:

- Begin tracing at the battery positive terminal.
 - Follow the complete path of current through each branch of the circuit.
 - Consider how current reaches each load and how it returns to the source.
 - Understanding current flow is an important troubleshooting skill.
 - Think about how a failure in one component would affect the rest of the circuit.
-
- Which component is the power source?
 - Which component provides circuit protection?
 - Which component controls current flow?
 - What are the two loads?
 - What type of circuit is shown?
 - Why do both lamps illuminate when the switch closes?

Optional Failure Scenarios:

- What happens if the fuse opens?
- What happens if the switch remains open?
- What happens if the headlight (L1) fails open?
- What happens if the indicator lamp (L2) fails open?
- What happens if the ground connection to L1 is lost?

Key Takeaway:

A parallel circuit provides multiple paths for current flow. A failure in one branch does not necessarily affect the operation of the other branches.


Module 4 – Circuit Components & Architecture

Activity

Trace the Circuit

Directions

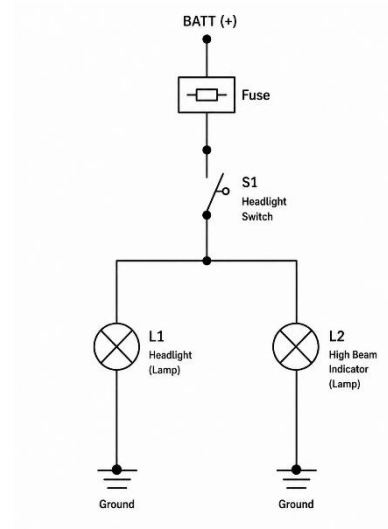1. Start at the battery positive terminal.
2. Trace the path current follows when switch S1 is closed.
3. Label the following components on the diagram:
 - Power Source
 - Protection Device
 - Control Device
 - Load #1
 - Load #2
 - Return Path
4. Answer the questions below.




Enlarged diagram on next page

Questions

- Which component provides power to the circuit? _____
- Which component protects the circuit from excessive current? _____
- Which component controls current flow? _____
- What are the two loads in this circuit? _____
- What type of circuit is shown? Series Parallel
- Why do both lamps illuminate when the switch closes? _____

(Optional) Troubleshooting Challenge

Failure Condition	What Happens?
Fuse opens	
Switch remains open	
Headlight (L1) fails open	
Indicator lamp (L2) fails open	
Ground connection to L1 fails	

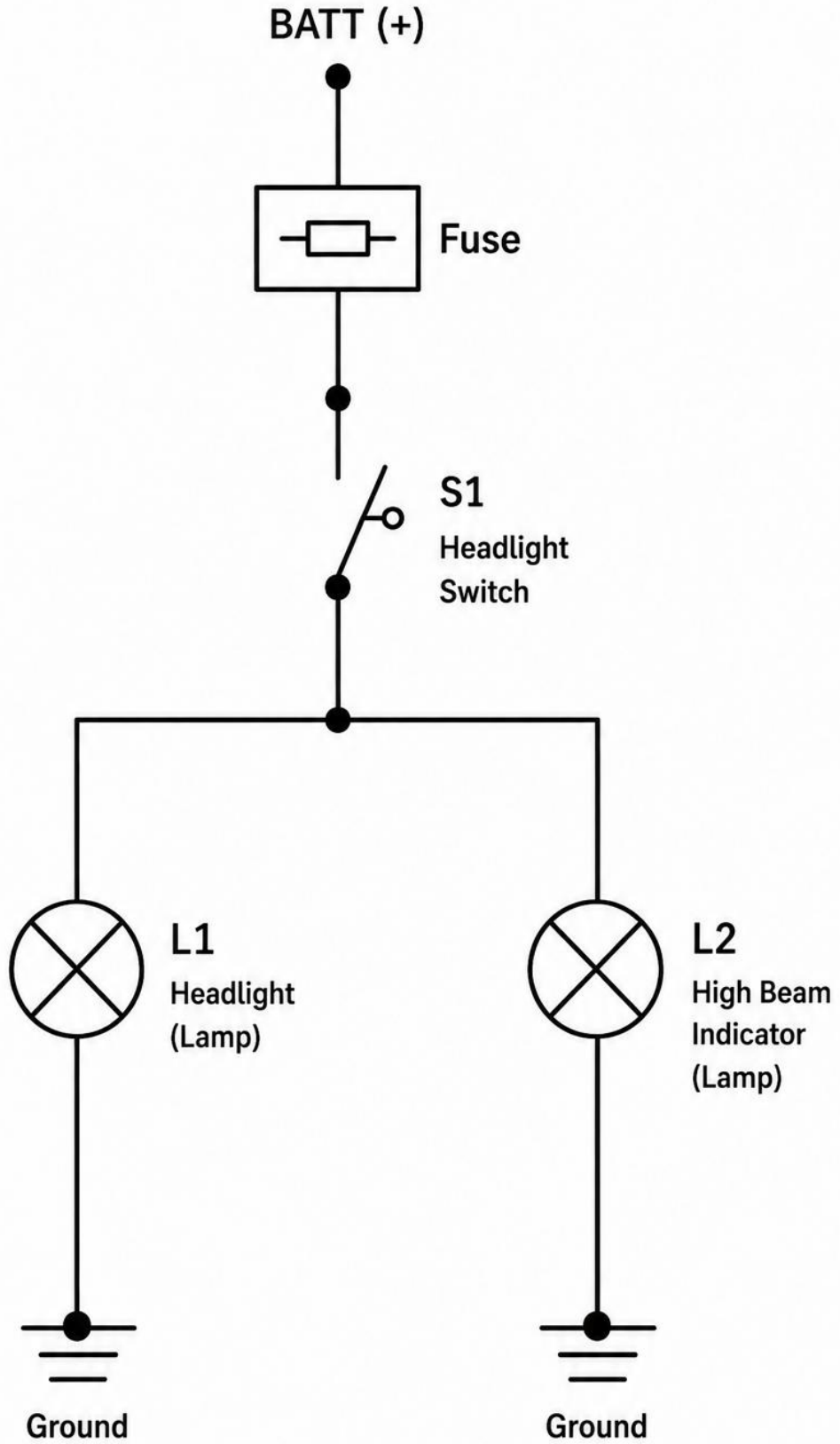

Knowledge Check



What does this image represent?



A.) Schematic

B.) One-Line Diagram

C.) Block Diagram


D.) Tempered-Fit Diagram

98

Activity: Building Circuits

Working in small groups:

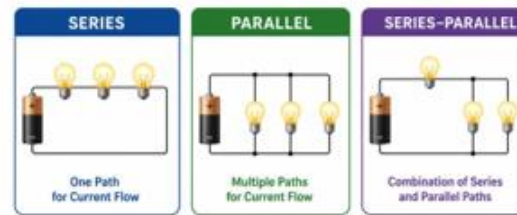- Build a series circuit
- Build a parallel circuit
- Build a series parallel circuit
- Test each circuit and observe what happens when a bulb is removed.
- Record your observations on the activity sheet in your binder.



99

Notes:

Review Questions:

- What characteristics define a series circuit?
- What characteristics define a parallel circuit?
- What makes a circuit series-parallel?
- What happened when a bulb was removed from each circuit?
- Which circuit architecture provides the greatest reliability?
- Why are parallel circuits commonly used in transit vehicles and equipment?

Key Takeaways

- A **series circuit** contains a single path for current flow. If one component fails, the entire circuit is interrupted.
- A **parallel circuit** contains multiple current paths. Components can continue operating even if one branch fails.
- A **series-parallel circuit** combines characteristics of both configurations.
- Understanding circuit architecture is critical when reading diagrams and troubleshooting electrical systems.
- Many transit vehicle electrical systems utilize parallel branches to improve reliability and maintain operation of critical components.

Module 4 – Circuit Components & Architecture

Summary and What's Next


- ✓ Electrical diagrams are maps of how a system is put together.
- ✓ Block diagrams show major systems and how they connect.
- ✓ One-line diagrams show how power is distributed.
- ✓ Schematics show how components are connected in a circuit.

100

Notes:

- Electrical diagrams are essentially maps. They show how a system is organized and how its parts are connected.
- We discussed **block diagrams**, which give a general, high-level view. They show major systems and how they *connect* to one another, but not the internal details.
- We looked at **one-line diagrams**, which simplify how electrical *power is distributed* throughout a system.
- And we reviewed **schematics**, which show the detailed *connections* between individual components in a circuit.
- Each type of diagram serves a different purpose — from big-picture system layout to detailed troubleshooting.
- The **key takeaway** is this: Understanding what type of diagram you're looking at determines how you interpret the information.
- Now that you understand the different diagram types, the next step is learning the language they use.
- Next, we'll focus on the symbols used to draw and read these diagrams — because being able to recognize symbols is essential for working in the field.

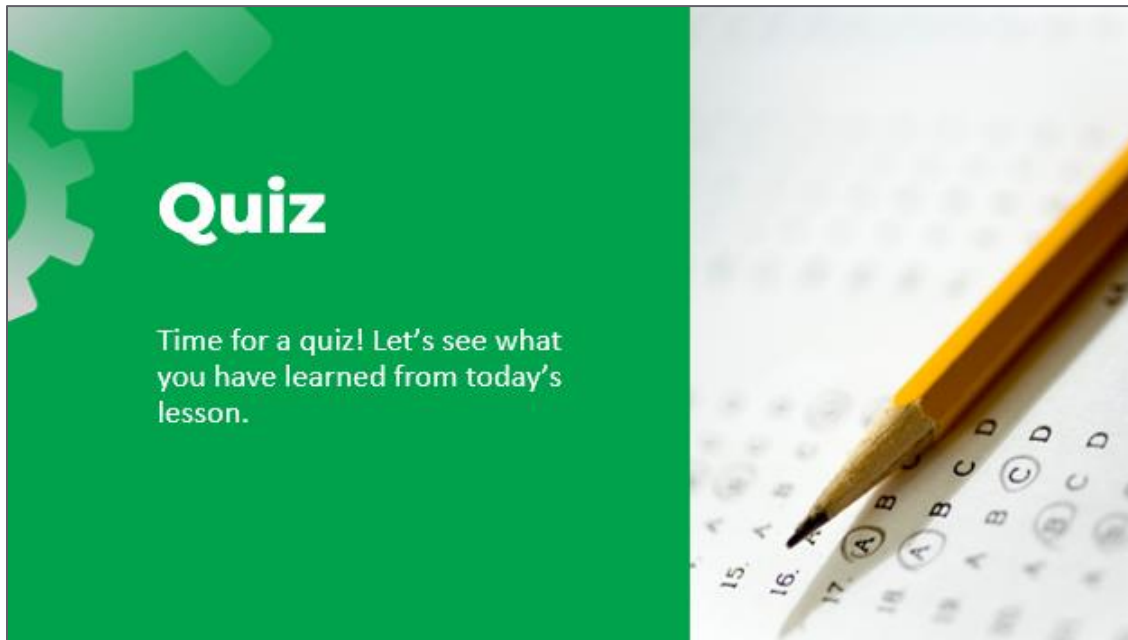Module 4 – Circuit Components & Architecture



Notes:

- Time for a quiz! Let's see what you have retained from today's lesson.

Revisiting the Objectives

- Define basic types of circuits and differences between them.
- Draw and label a simple electrical circuit.
- Define the major components of an electrical circuit and describe their functionality
- Apply Kirchhoff's Current and Voltage Laws to analyze circuits and solve for unknown electrical values.
- Identify the major symbols for circuit components.
- Recognize basic electrical diagrams

102

Notes:

- If you were explaining today's objectives to someone else, how would you summarize what they mean and why they matter?
- Which of today's objectives do you feel most confident about? Which were most challenging? Explain your reasoning.
- Can you give an example of how you could apply one of today's objectives in a real-world situation?
